
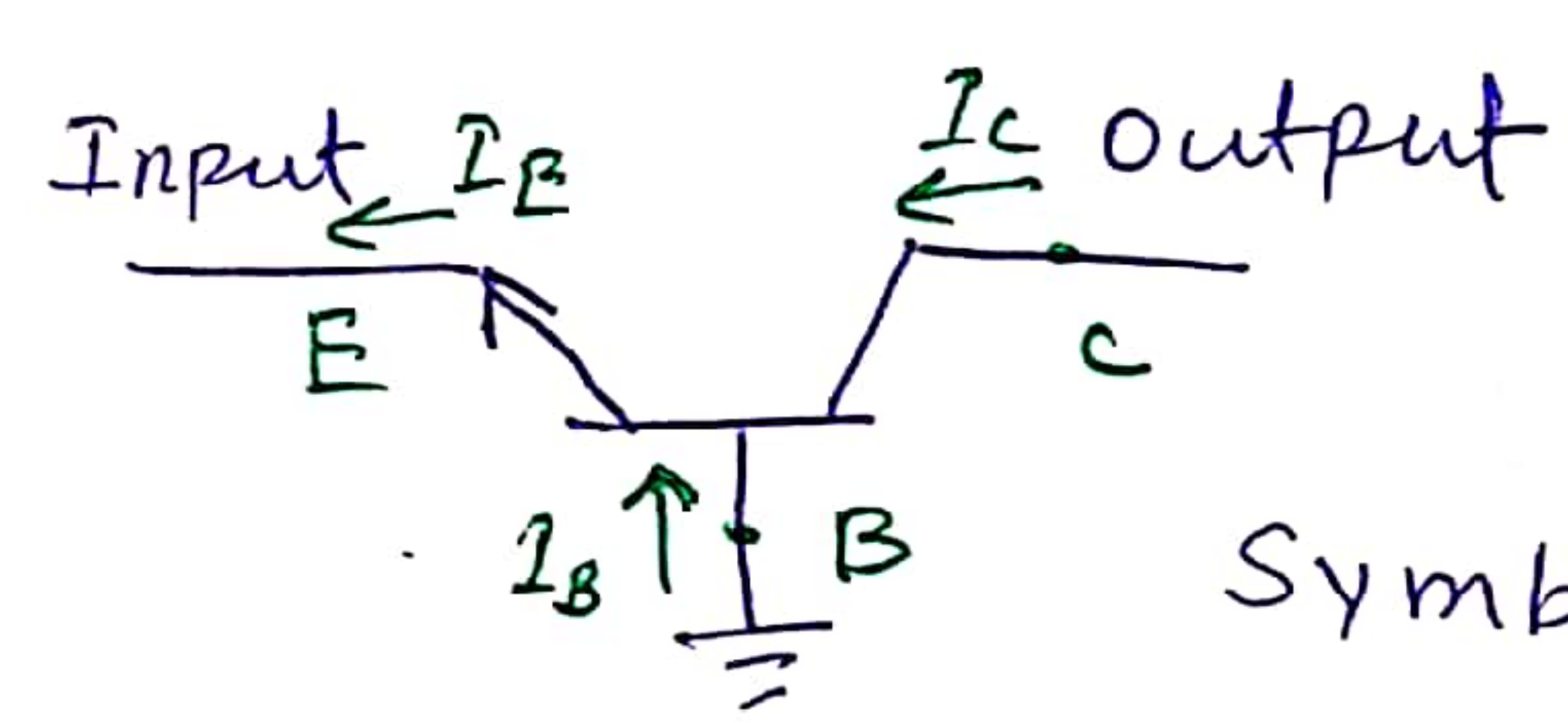


BJT CONFIGURATIONS AND CHARACTERISTICS :

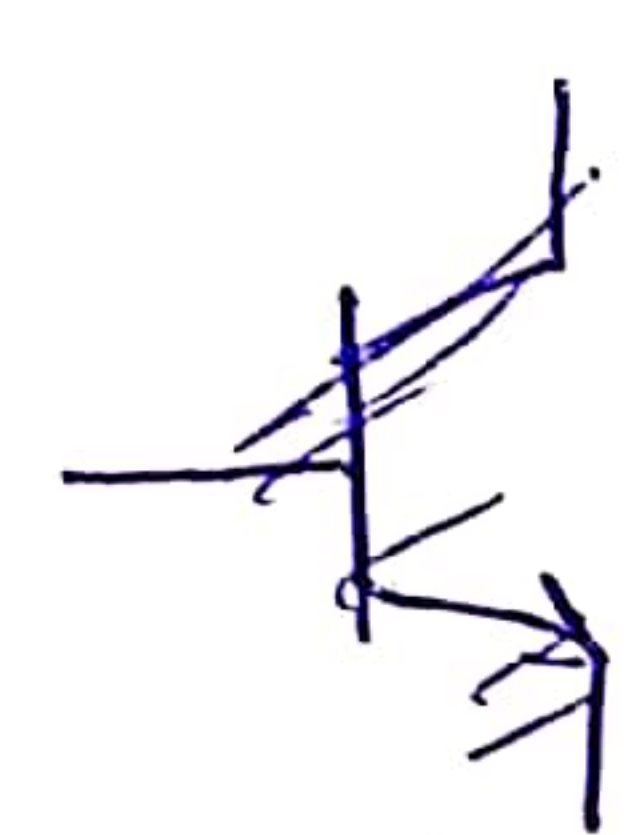- BJT is generally operated in three different Characteristics.
 - (i) Common-Base
 - (ii) Common-Emitter
 - (iii) Common collector
- Common-Base means that the Base-terminal is common to both input & output and so on.
- Each Configuration have two characteristics - Input & output
- (1) Common-Base Configuration :-
(C.B. config.)



Symbolic representation

(npn as a CB config.)

Known as CB Current gain

$$\alpha = \frac{I_C}{I_E}$$

Output Characteristics



I_C Vs V_{CB}

The o/p characteristics plot the o/p current I_C versus output voltage V_{CB} for various value of I_E .

Input Characteristics

I_E Vs V_{BE}

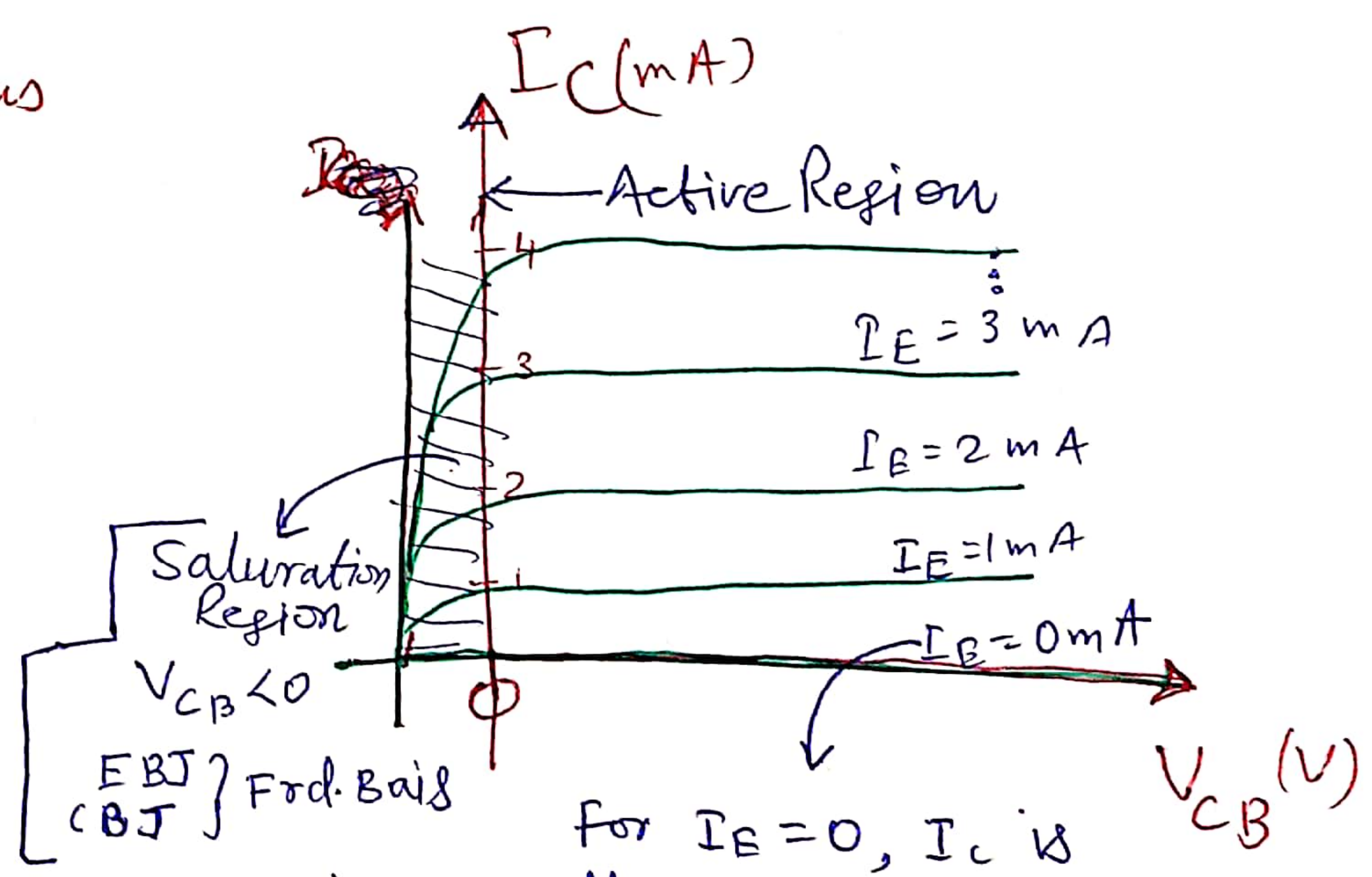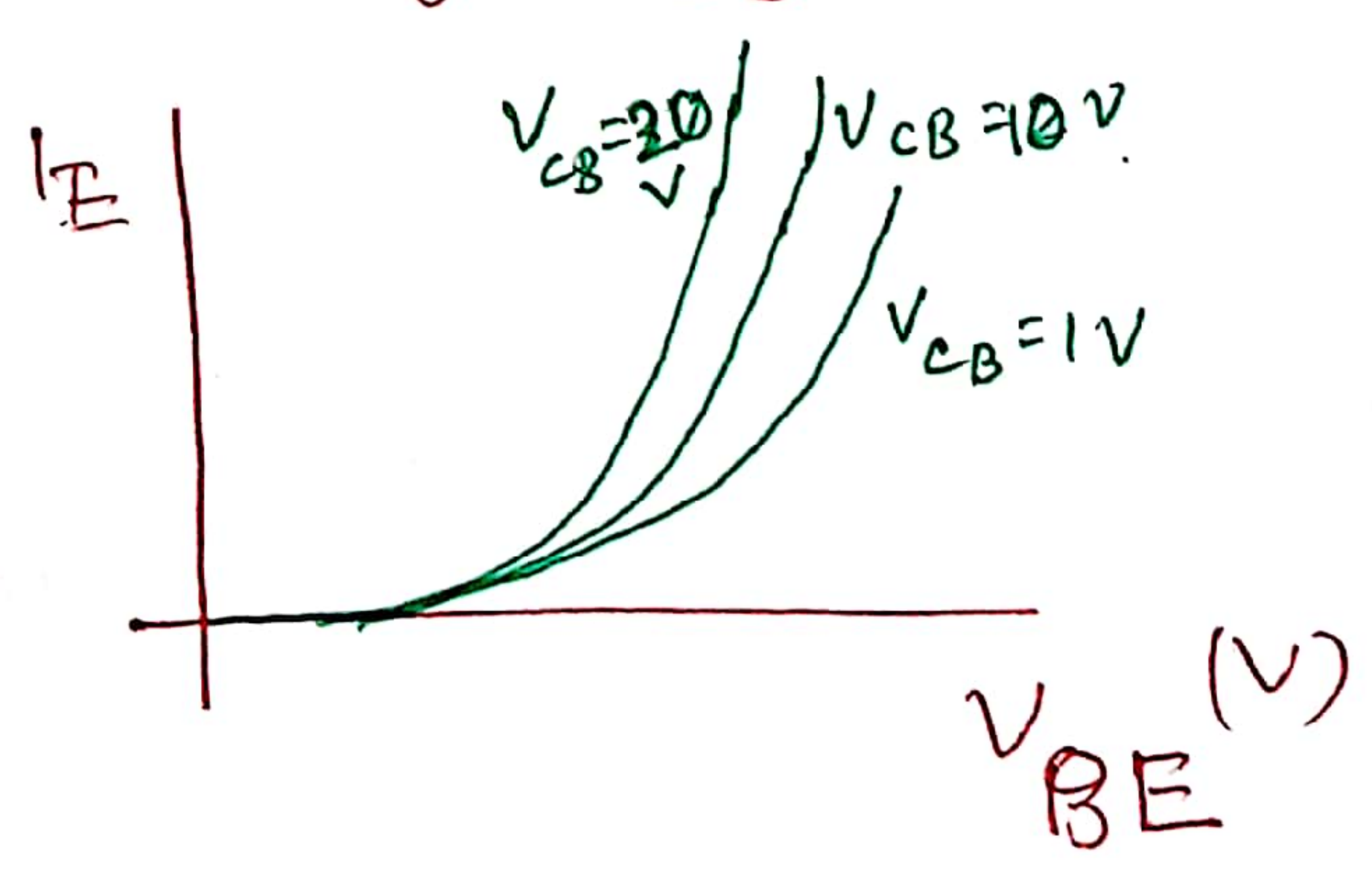
The characteristics represent input current, I_E to and input voltage, V_{BE} for various value of V_{CB}



For $I_E = 0$, I_C is very small simply that due to reverse saturation current, I_{CO}

$I_{CBO} \Rightarrow$ Rev. Saturation current

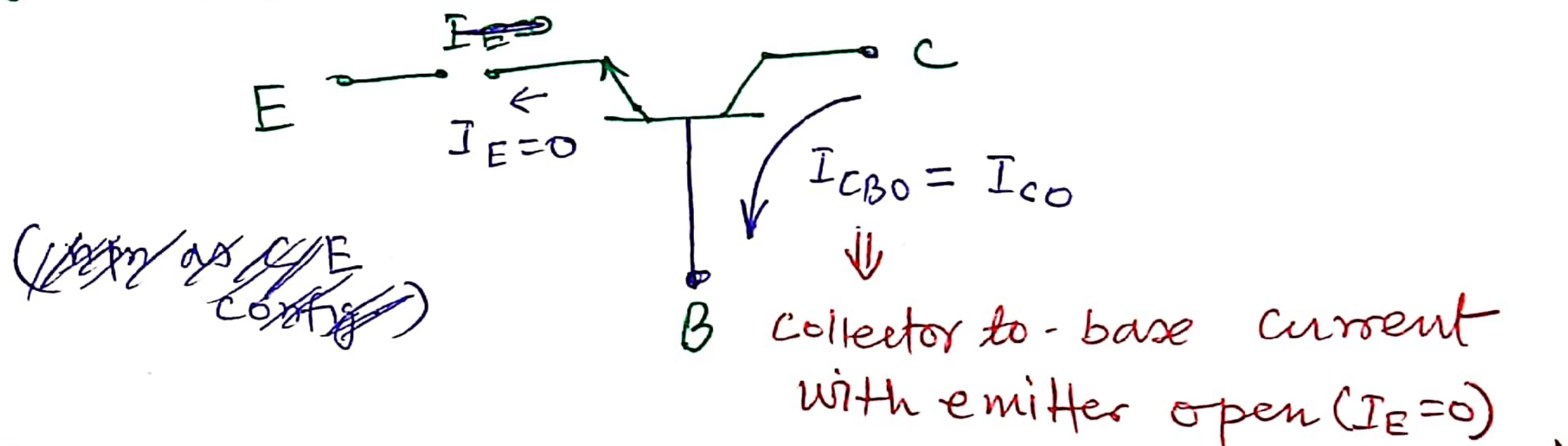I_C for ($I_E = 0$) is known as Rev. Saturation current and for common-base configuration, it is denoted by I_{CBO}



The I_C can be defined as


$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (1)}$$

$\alpha \approx 1$ (slightly less than 1, as defined earlier)



For From this eqn., for $I_E = 0$, $I_C = I_{CBO}$

(II) Common Emitter Configuration (CE) :-

Emitter is common to both i/p & o/p

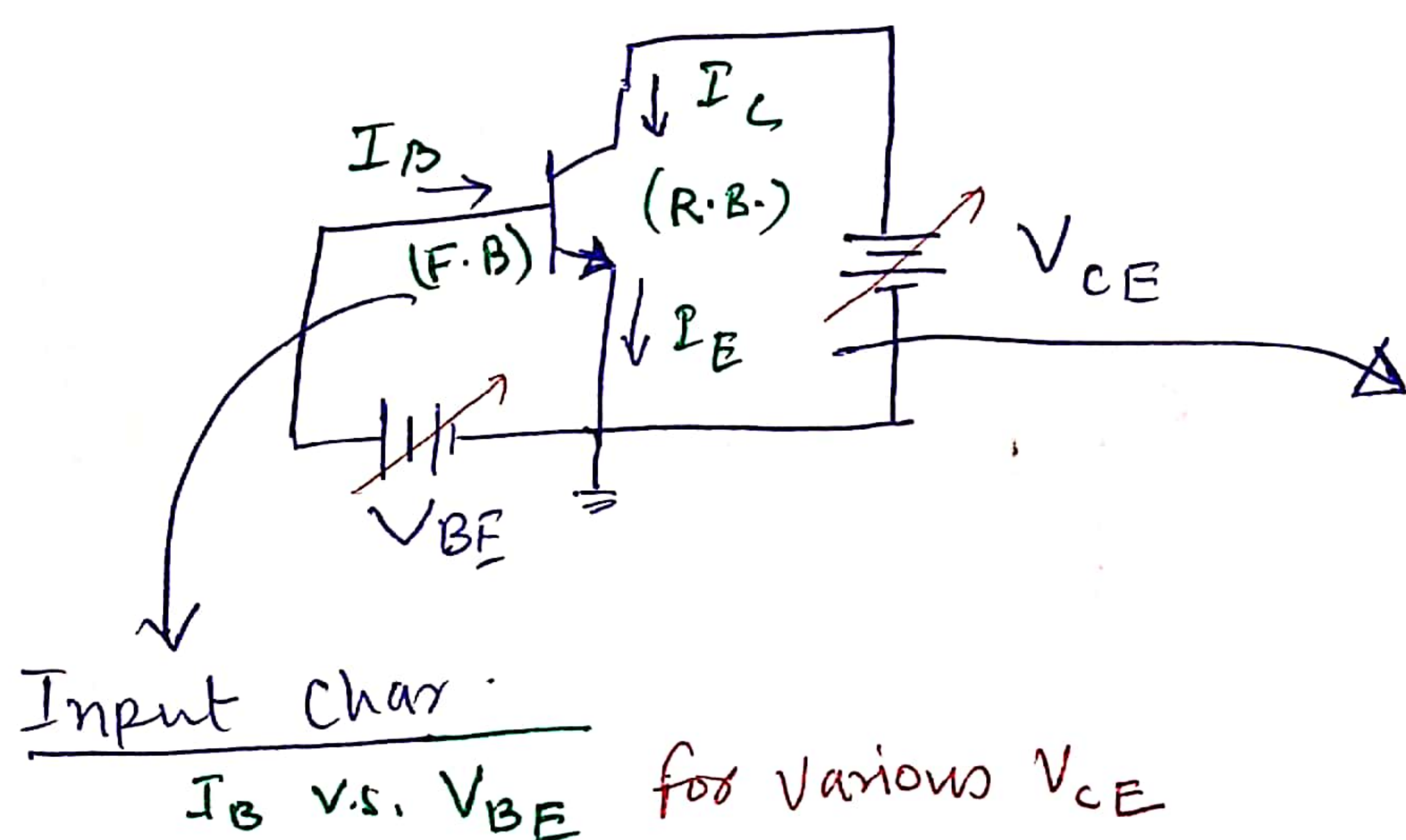


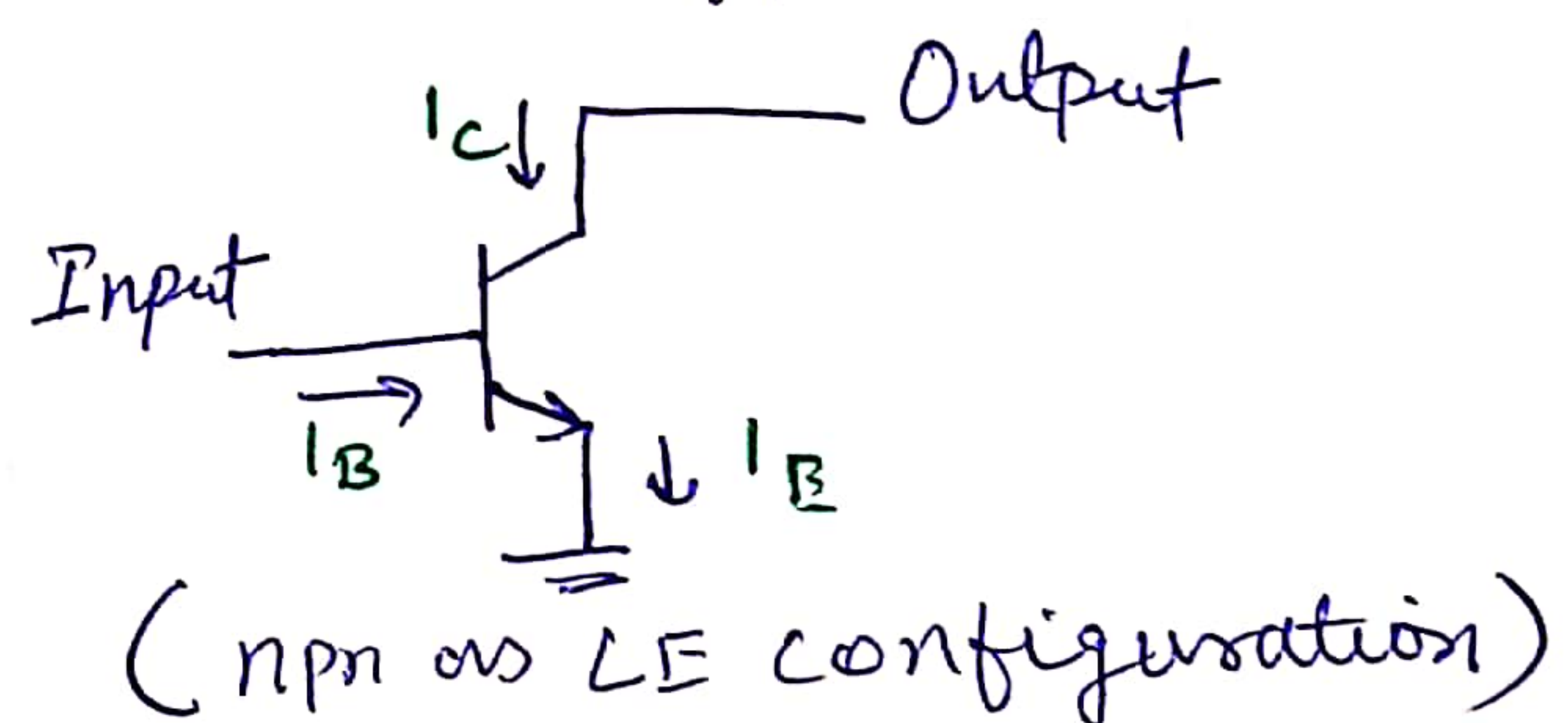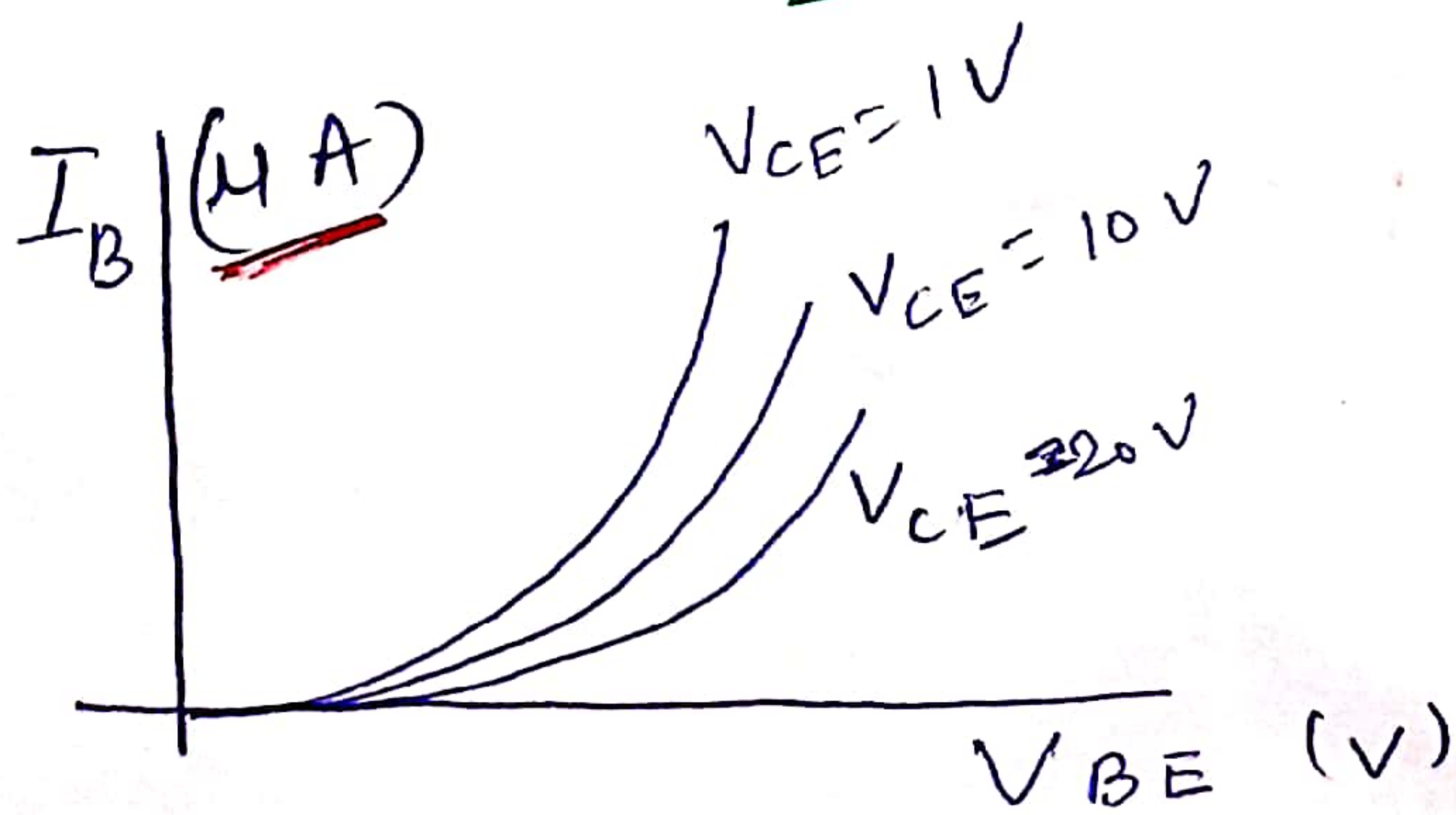Input Char.
 I_B vs. V_{BE} for various V_{CE}



(npn as CE configuration)
Output characteristic

I_C vs V_{CE} for various I_B

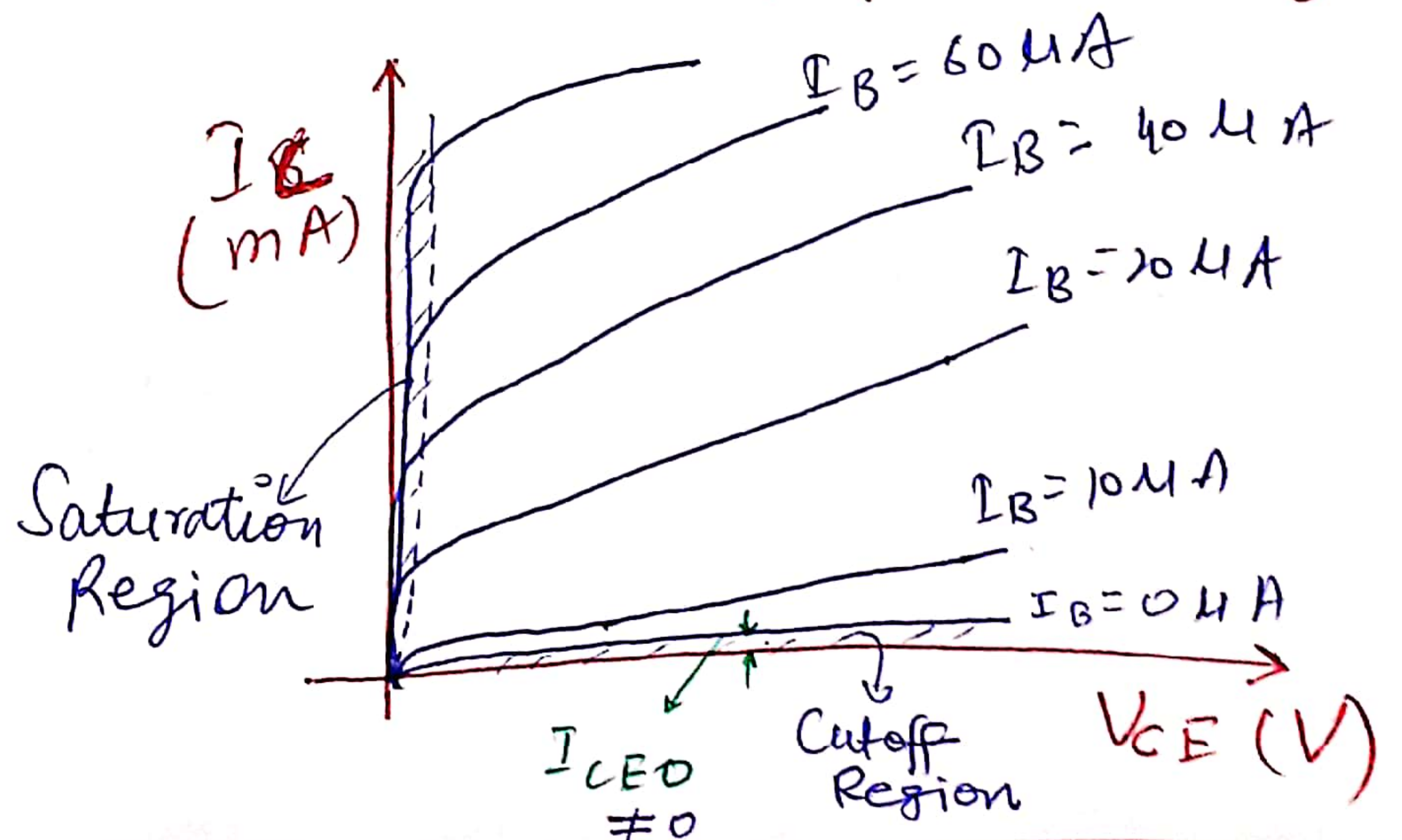

- (5)
- The base current are very small and have the unit of μA .
 - We ^{can} observe from the o/p characteristic that for $I_B = 0 \mu A$ I_C is not near to zero, it has some positive value, known as I_{CEO}

Using Eq (1)

$$I_C = \alpha I_E + I_{CBO}$$


Putting $I_E = I_C + I_B$

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + \frac{I_{CBO}}{1-\alpha}$$

$$= \beta I_B + \frac{I_{CBO}}{1-\alpha}$$

$$I_C = \beta I_B + I_{CEO}$$

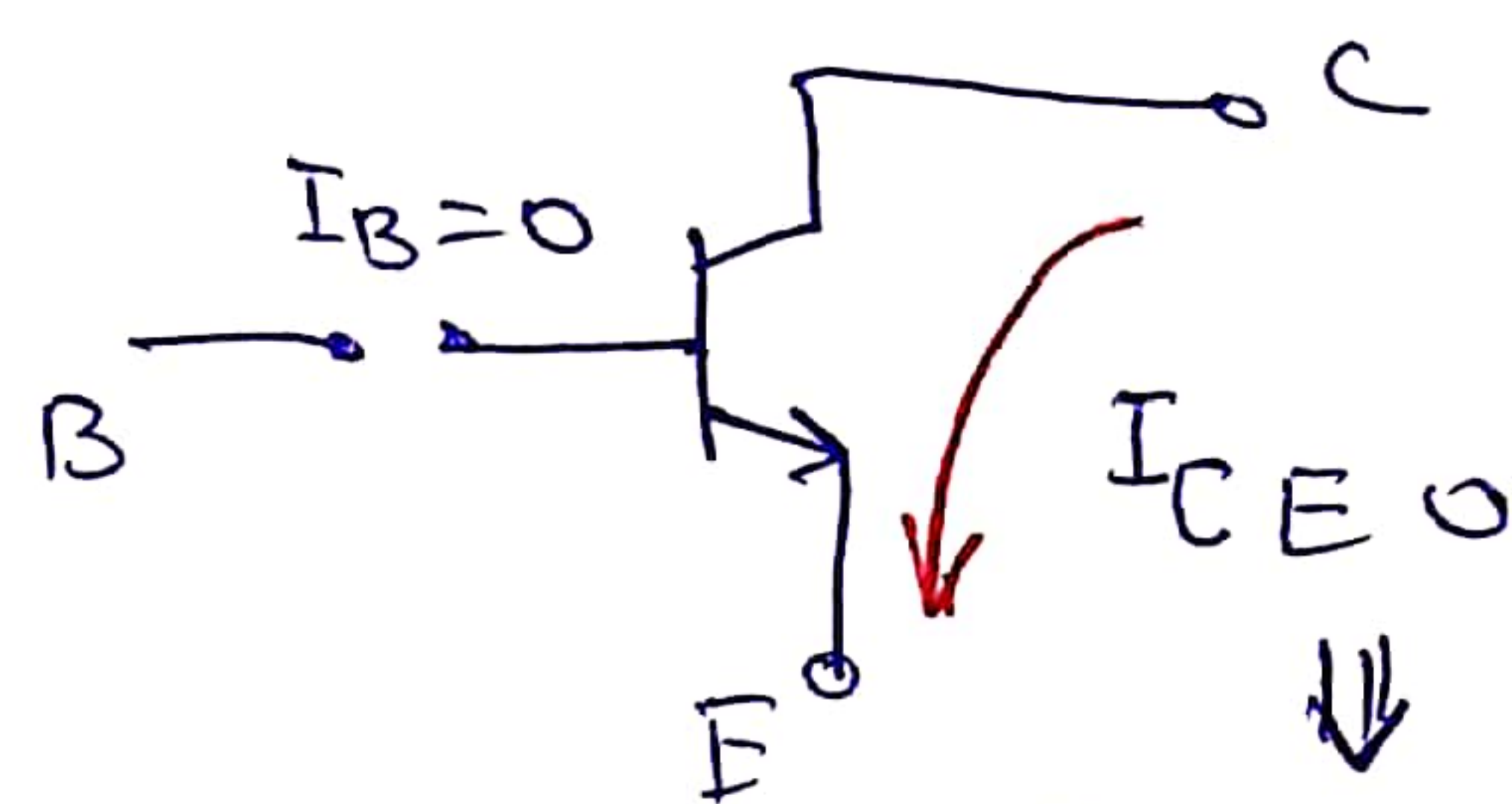

Collector to emitter current with Base open ($I_B = 0$)

Since $\frac{\alpha}{1-\alpha} = \beta$

where

$$I_{CEO} = \frac{I_{CBO}}{1-\alpha} \Big|_{I_B=0}$$

For $\alpha = 0.98$ & $I_{CBO} = 1 \mu A$
 $I_{CEO} = \underline{50 \mu A}$

$$I_{CEO} = \frac{I_{CBO}}{1-\alpha}$$

$$I_{CEO} = (\beta + 1) I_{CBO}$$

Since, $\frac{\alpha}{1-\alpha} = \beta$

$$\frac{\alpha}{1-\alpha} + 1 = \beta + 1$$

$$\frac{1}{1-\alpha} = \beta + 1$$

* CE current gain

' β ' is known as CE current gain

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$\beta: 100-200$$

