

# UNIT :4

## COMBINATIONAL CIRCUITS


# LOGIC CIRCUITS

2

- 2.1 Multiplexers (MUX)
- 2.2 Decoders
- 2.3 Encoders
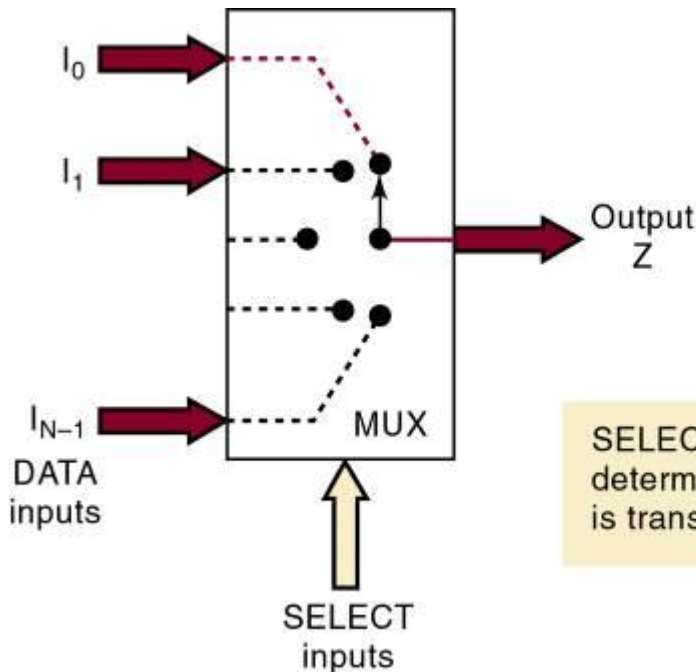
## 2.1) Multiplexers (Data Selectors)

- A **multiplexer (MUX)** selects 1 of  $N$  input data sources and transmits the selected data to a single output—called **multiplexing**.
  - ▣ Basic function: select one of its  $2^N$  data input lines and place the corresponding information onto a single output line.




Routing control of desired data input to output by SELECT inputs—referred to as ADDRESS inputs.

SELECT input code determines which input is transmitted to output Z.

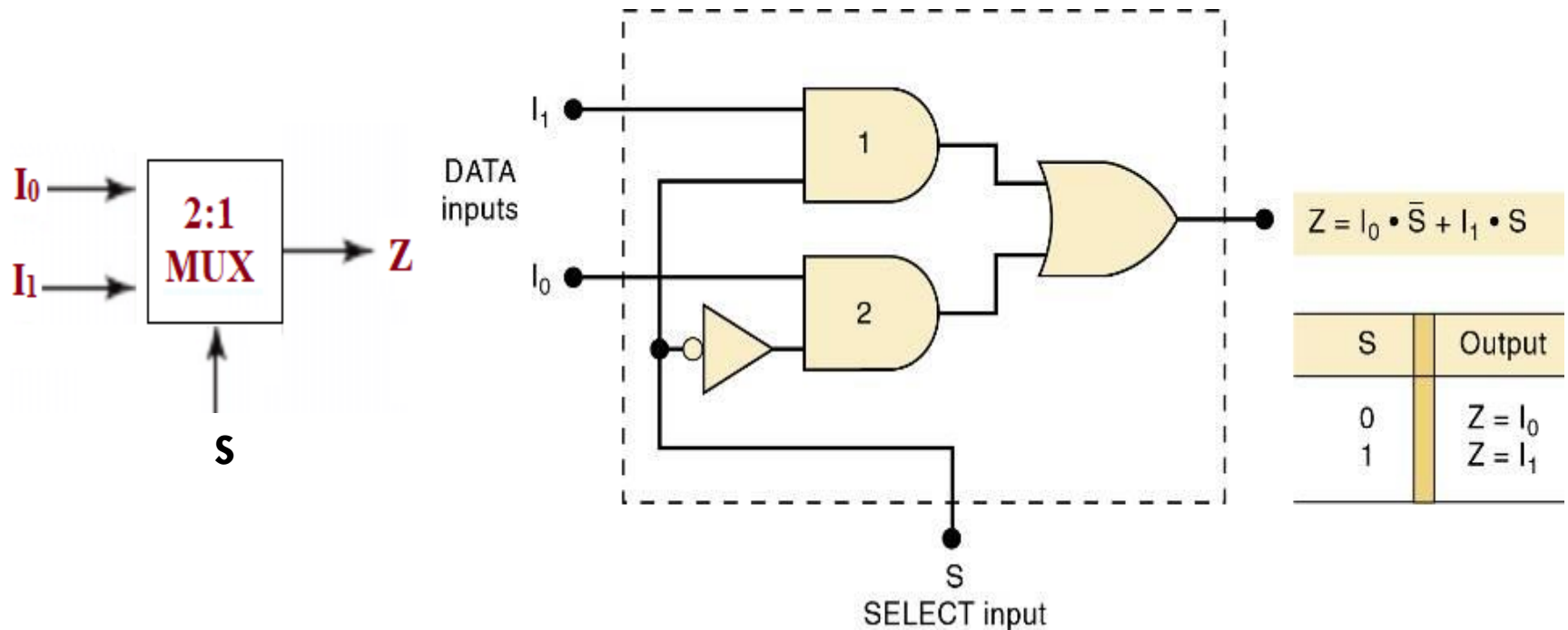
# 2-1 Multiplexer

- A two-input MUX comprises of 2 Data Input's  $I_0$  &  $I_1$
- It comprises of a single Select Input  $S$
- Based on the value of  $S$  (either 0/1), either the value of  $I_0$  or  $I_1$  is transferred at the output




# Logic Symbol of 4-1 Multiplexer

5

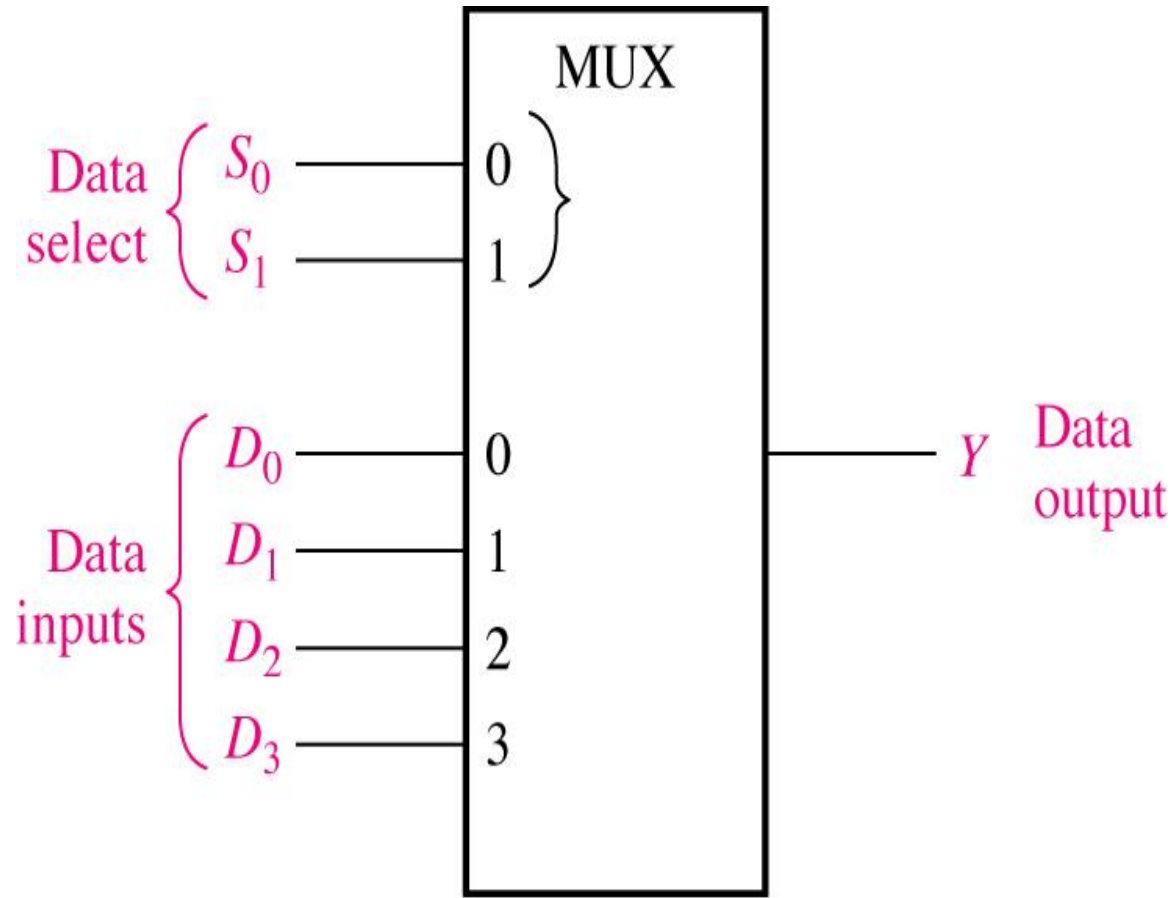
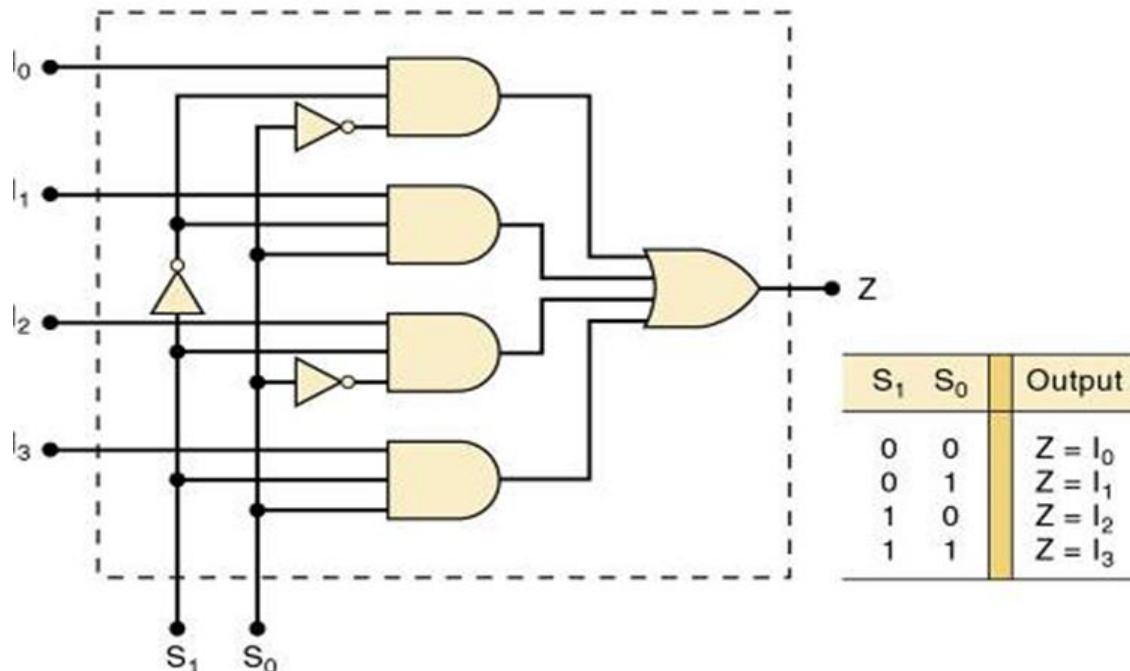
# 4-1 Multiplexers (Data Selectors)


- Four Input Multiplexer comprises of 4 Data Inputs & 2 Select Input lines
  - Based on the combination of select inputs, either of the data input is transferred to the output.


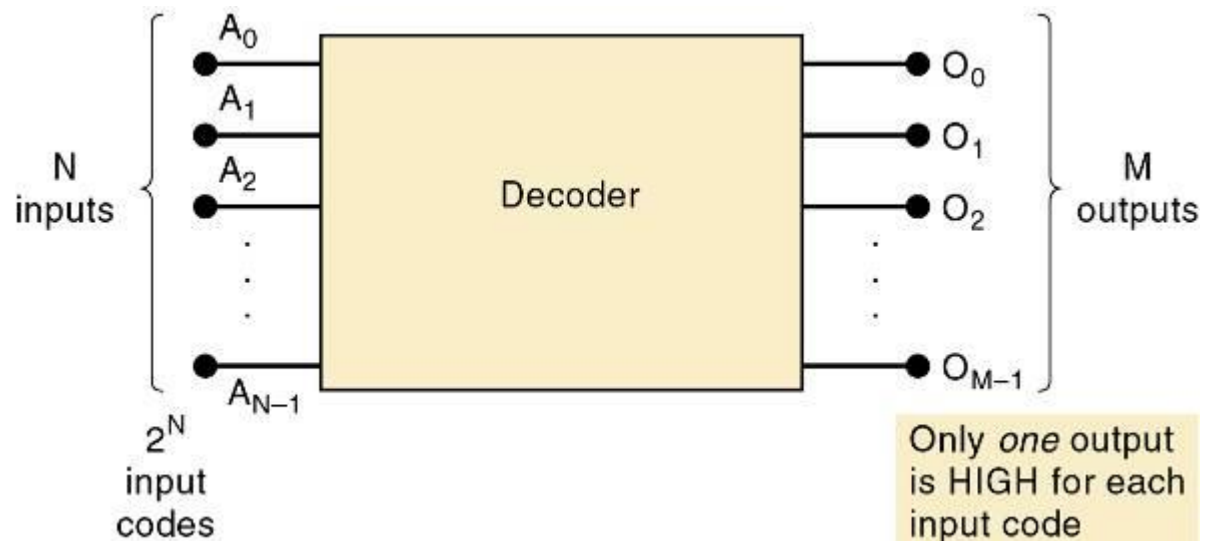
## 2.2) Decoders

- A **decoder** accepts a set of inputs that represents a binary number—activating only the output that corresponds to the input number.

For each of these input combinations, only one of the  $M$  outputs will be active (HIGH); all the other outputs are LOW.




Many decoders are designed to produce active-LOW outputs, where only the selected output is LOW while all others are HIGH.
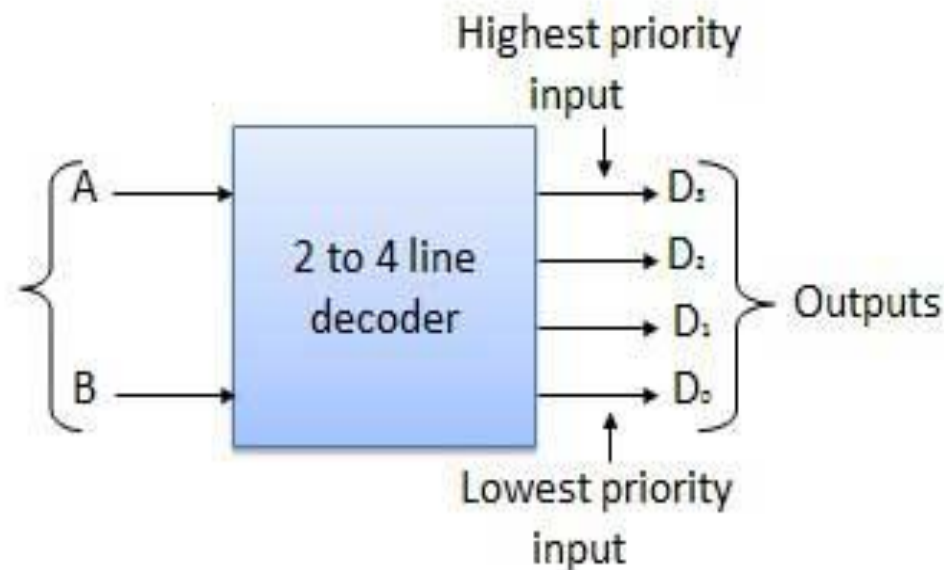
# 2 line to 4 line Decoder

8

- Block diagram of 2-line to 4-line Decoder comprising of 2 Inputs & 4 Outputs is shown in the figure.





# 2 line to 4 line Decoder

9

- When  $A = 0$  &  $B = 0$ , Output  $D_0$  is activated (Logic 1), remaining all outputs are deactivated (Logic 0)
- When  $A = 0$  &  $B = 1$ , Output  $D_1$  is activated (Logic 1), remaining all outputs are deactivated (Logic 0)
- When  $A = 1$  &  $B = 0$ , Output  $D_2$  is activated (Logic 1), remaining all outputs are deactivated (Logic 0)
- When  $A = 1$  &  $B = 1$ , Output  $D_3$  is activated (Logic 1), remaining all outputs are deactivated (Logic 0)

INPUTS		OUTPUTS			
A (MSB)	B (LSB)	$D_3$ (MSB)	$D_2$	$D_1$	$D_0$ (LSB)
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

# 3 line to 8 line Decoder

10

- A 3 line to 8 line Decoder has 3 Inputs and 8 Outputs.
- Also called Binary to Octal Decoder-taking 3 bit binary input code and activating one of eight (octal) outputs
- Also referred to as a 1-of-a-8-Decoder-only 1 of the 8 outputs is activated at a time.

# 3 line to 8 line Decoder

11

- Truth Table of 3 line to 8 line Decoder is given below
- Assignment Question : Draw the block level diagram of 3 line to 8 line Decoder & explain the operation

A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

## 2.3) Encoders

- Most decoders accept an input code & produce a HIGH (or LOW) at *one and only one* output line.
  - ▣ A decoder identifies, recognizes, or detects a particular code.

## 2.3 ) Encoders


- The opposite of decoding process is **encoding**.
  - ▣ Performed by a logic circuit called an **encoder**.

An encoder has a number of input lines, only **one** of which is activated at a given time.

Shown is an encoder with  $M$  inputs and  $N$  outputs.

Inputs are active-HIGH, which means that they are normally LOW.

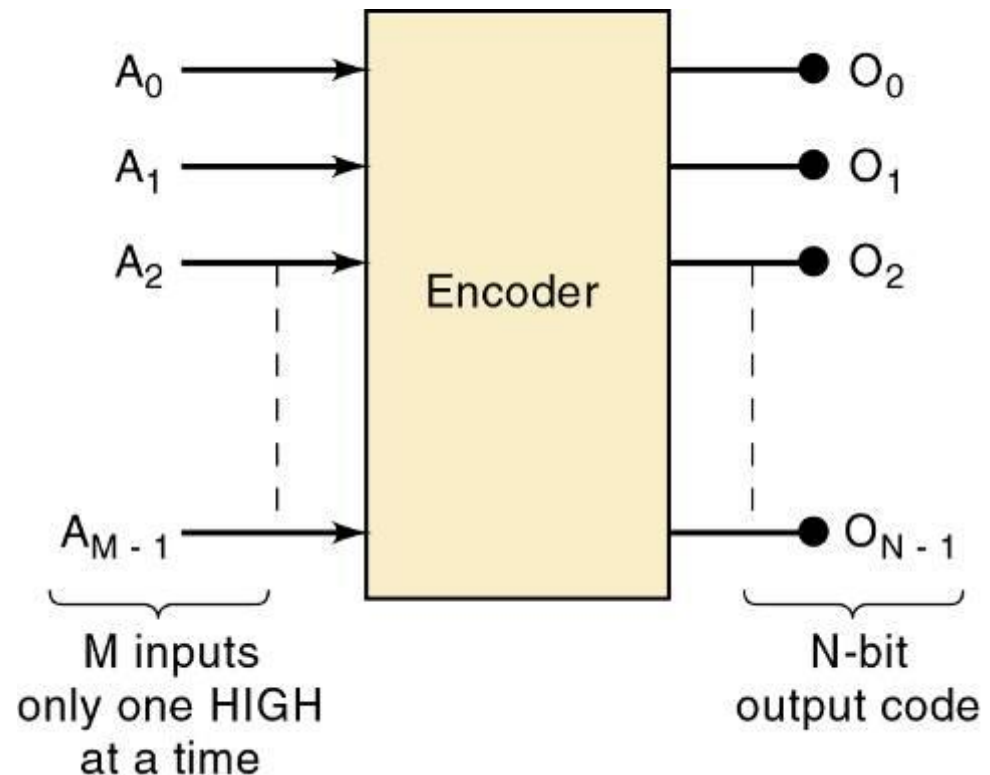It produces an  $N$ -bit output code, depending on which input is activated.




# 4 line to 2 line Encoder

14

- A 4 line to 2 line Encoder comprises of 4 Inputs and 2 Outputs.
- Based on the Input that's being activated a 2 bit code is generated at the output.
- The block diagram and truth table of the aforementioned is shown

# 4 line to 2 line Encoder

15

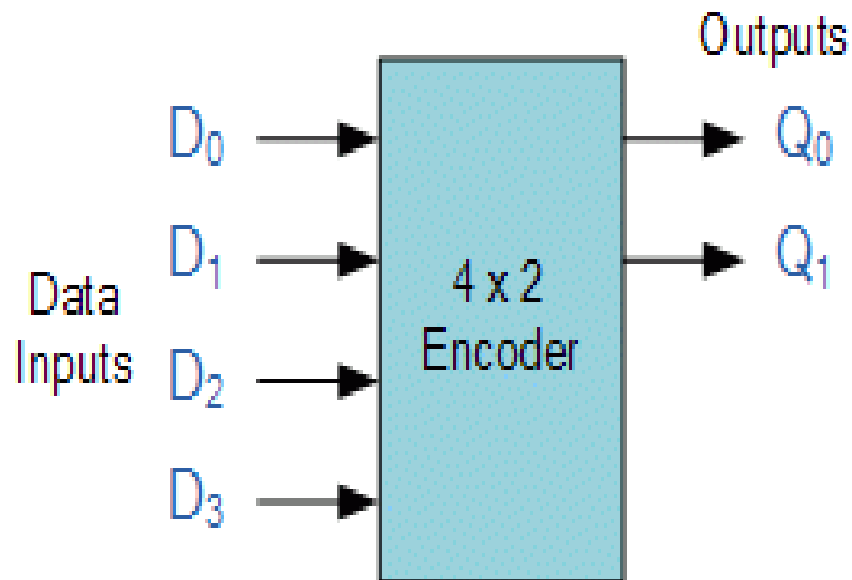

Inputs				Outputs	
$D_3$	$D_2$	$D_1$	$D_0$	$Q_1$	$Q_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x