



ELA – 2110

ELECTRONICS DEVICES AND CIRCUITS

HOME ASSIGNMENT 2

NAME: MOHD. ZAID ALI


FACULTY NO: 19COB103

ENROLL. NO: GL3125

HOME ASSIGNMENT


Q Find the small voltage gain and I/O impedance of common collector amplifier using hybrid- π model of transistor.

Soln:-

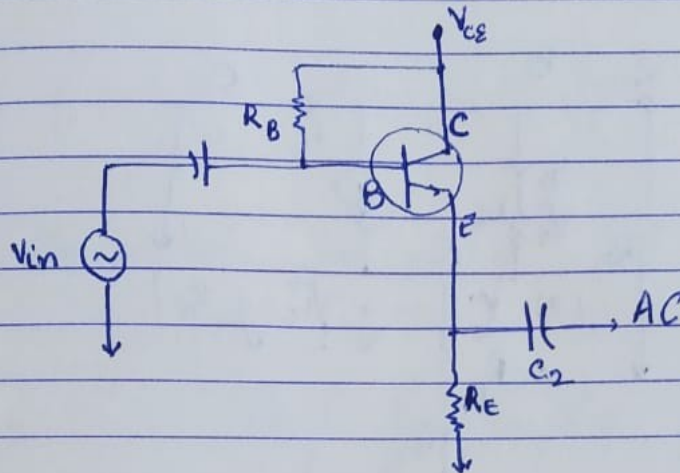


AC signal perspective \Rightarrow all DC signals being grounded and all Coupling Capacitors being short circuited.

Equivalent of AC:

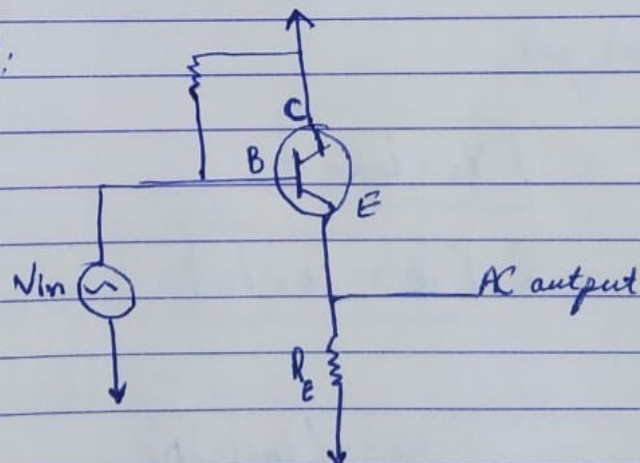

Small signal Analysis of Common Emitter BJT

Hybrid- π -Model

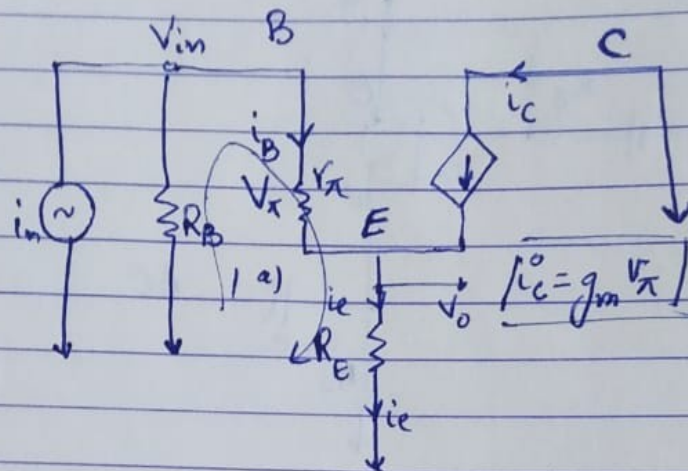

Calculating the voltage gain,

we get,

$$V_o = i_e R_E$$

$$\& i_e = i_B + i_c$$

\therefore

$$V_o = (i_B + i_c) R_E$$

we know,

$$V_{\pi} = i_B r_{\pi}$$

$$\therefore i_B = \frac{V_{\pi}}{r_{\pi}}$$

$$V_o = \left(\frac{V_{\pi}}{r_{\pi}} + i_c \right) R_E$$

\therefore we get,

$$V_o = V_x \left[\frac{1}{r_x} + g_m \right] R_E \quad \text{as } i_c = g_m V_x \quad \rightarrow (2)$$

Since,

$$\left| \frac{r_x = \beta}{g_m} \right| \Rightarrow \frac{1}{r_x} = \frac{g_m}{\beta}$$

on substitute $\frac{g_m}{\beta}$ in (2)

$$V_o = V_x \left[\frac{g_m}{\beta} + g_m \right] R_E \quad \frac{g_m}{\beta} \ll g_m$$

we can neglect it

$$\therefore \boxed{V_o = V_x [g_m] R_E} \quad - (3)$$

Applying KVL in (a)

$$\begin{aligned} V_{in} - V_x &= V_o \\ \therefore \boxed{V_{in} = V_o + V_x} \quad - (4) \end{aligned}$$

Substituting V_x from (4) in (3)

$$V_o = (V_{in} - V_o) [g_m] R_E$$

$$\therefore V_o + g_m R_E V_o = V_{in} g_m R_E$$

$$V_o [1 + g_m R_E] = V_{in} g_m R_E$$

Voltage gain

$$= \frac{V_o}{V_{in}} =$$

$$\frac{g_m R_E}{1 + g_m R_E} \Rightarrow \left[\frac{R_E}{\frac{1}{g_m} + R_E} \right]$$


Since

$$g_m \ll R_E, \text{ hence } A_v (\text{voltage gain}) \approx \frac{R_E \approx 1}{R_E}$$

Since no negative signs therefore Input-Output signals are in phase.

For Output Impedance:

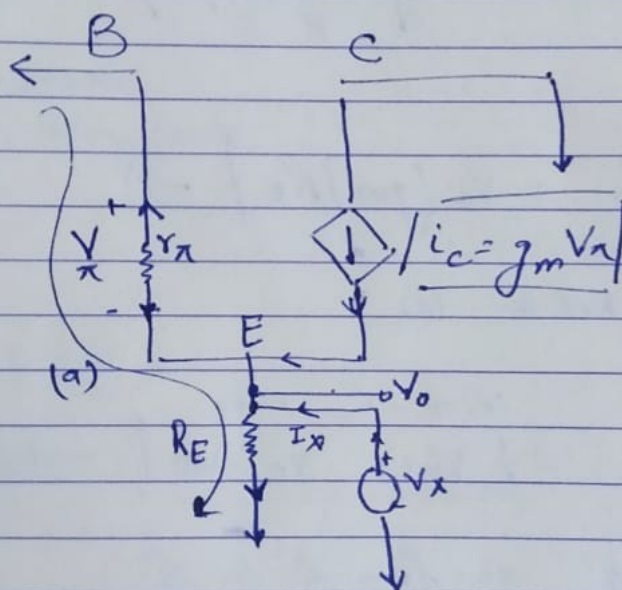On shortcircuit all independent sources and Resistor, Eq ckt, we get,



$$\left| \frac{V_x}{I_x} = Z_o \right| \text{ (output Impedance)}$$

Applying KCL at E junction,

$$\frac{V_x}{R_\pi} + \frac{V_x}{R_E} = I_x + i_c$$

$$\frac{V_x}{R_\pi} + \frac{V_x}{R_E} = I_x + g_m V_\pi \quad \& \quad |V_\pi = -V_x| \text{ from KVL in } \text{---}$$

$$I_x - g_m \frac{V_x + V_{x'}}{R_E} = I_x - g_m V_x$$

$$I_x = \frac{V_x}{R_E} + \frac{V_x}{r_{\pi}} + g_m V_x$$

$$I_x = V_x \left[\frac{1}{R_E} + \frac{1}{r_{\pi}} + g_m \right]$$

$$\left| \frac{I_x}{V_x} = \frac{1}{R_E} + \frac{1}{r_{\pi}} + g_m \right|$$


$$\& \frac{1}{r_{\pi}} \ll g_m$$

\therefore

$$\left| \frac{I_x}{V_x} = \frac{1}{R_E} + g_m \right|$$

$$\Rightarrow \left| R_o = \frac{1}{\frac{1}{R_E} + g_m} \right| \quad \text{ie } \frac{1}{R_E} \text{ in parallel with } g_m$$

for Input Impedance:

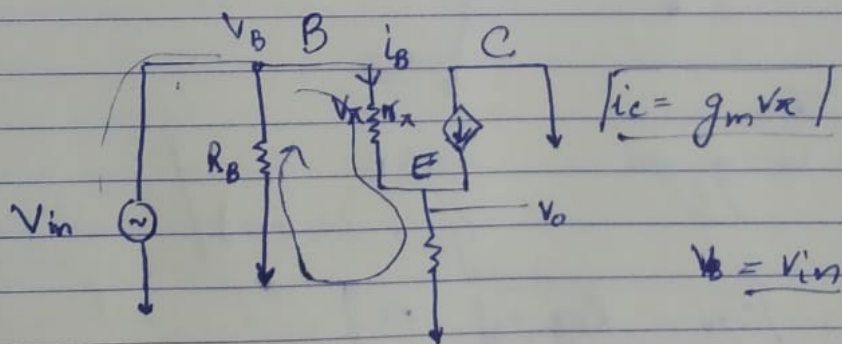


$$\left| V_B = V_{\pi} + V_E \right|$$

$$V_B = i_B r_{\pi} + (\beta + 1) i_B R_E$$

$$\left| \frac{V_B}{i_B} = r_{\pi} + (\beta + 1) R_E = Z_B \right|$$

Egt. ckt:

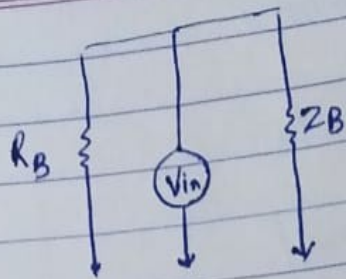


$$Z_{in} = R_B \parallel Z_B$$

$$\frac{1}{Z_{in}} = \frac{1}{R_B} + \frac{1}{Z_B} \Rightarrow \frac{1}{R_B} + \frac{1}{r_{\pi} + (\beta+1)R_E}$$

So, $Z_B =$

$$Z_B = r_{\pi} + (\beta+1)R_E$$

If for a finite output resistance,

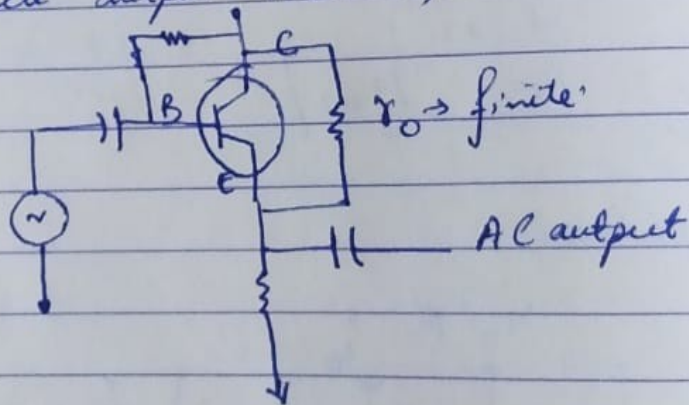

Then,

$$\text{Voltage gain} = \frac{R_E \parallel r_o}{\frac{1}{g_m} + (R_E \parallel r_o)}$$

$$Z_{in} = R_B \parallel Z_B \Rightarrow \frac{1}{R_B} + \frac{1}{r_{\pi} + (\beta+1)(R_E \parallel r_o)}$$

$$\therefore Z_o = \left(\frac{1}{g_m} \right) \parallel (R_E \parallel r_o)$$