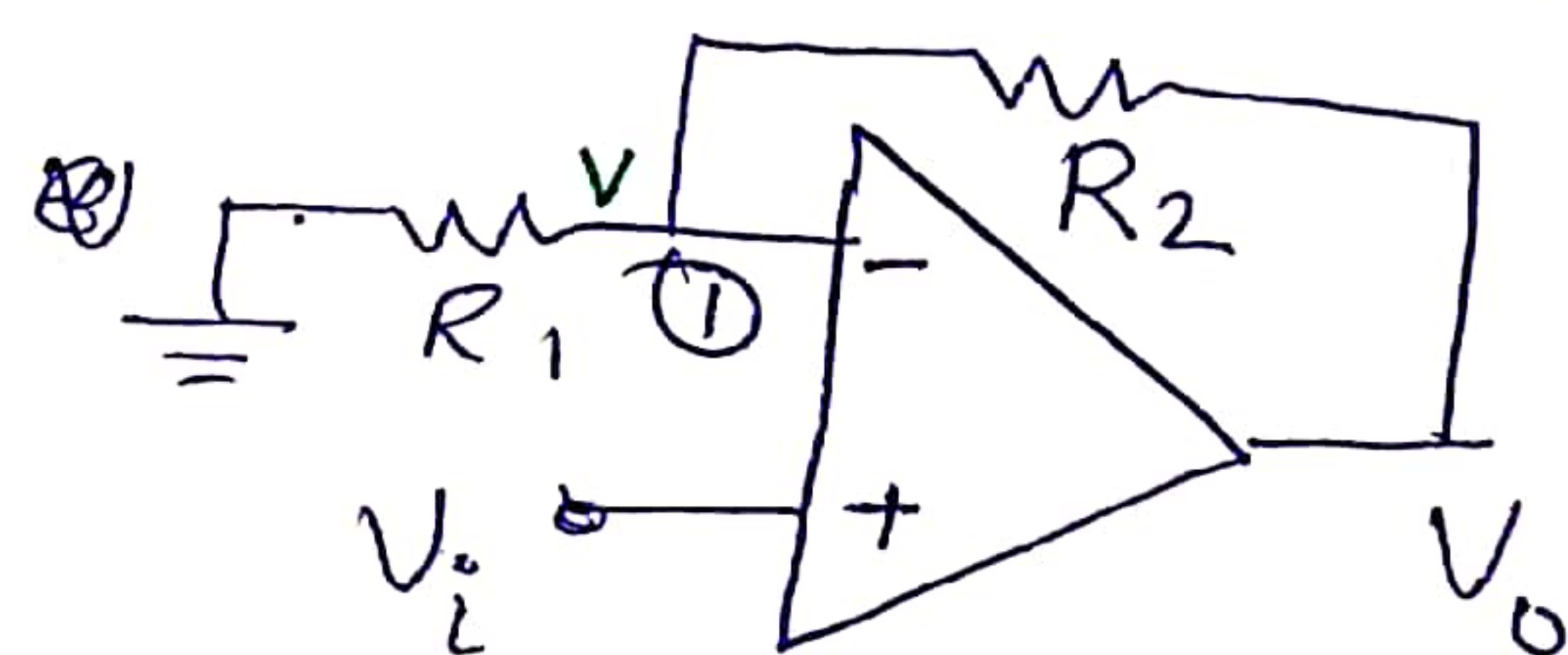


## Non-Inverting Amplifier Configuration :

(Input is applied at non-inv input terminal)



Writing nodal eqn at ①, let the voltage at ~~node~~ ① be  $V$

$$V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = 0 \times \frac{1}{R_1} + V_o \times \frac{1}{R_2}$$


But due to V.S.C.,  $V = V_i$

$$V_i \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_o}{R_2}$$

Or,

$$\boxed{V_o = \left( 1 + \frac{R_2}{R_1} \right) V_i} \quad \text{--- (1)}$$

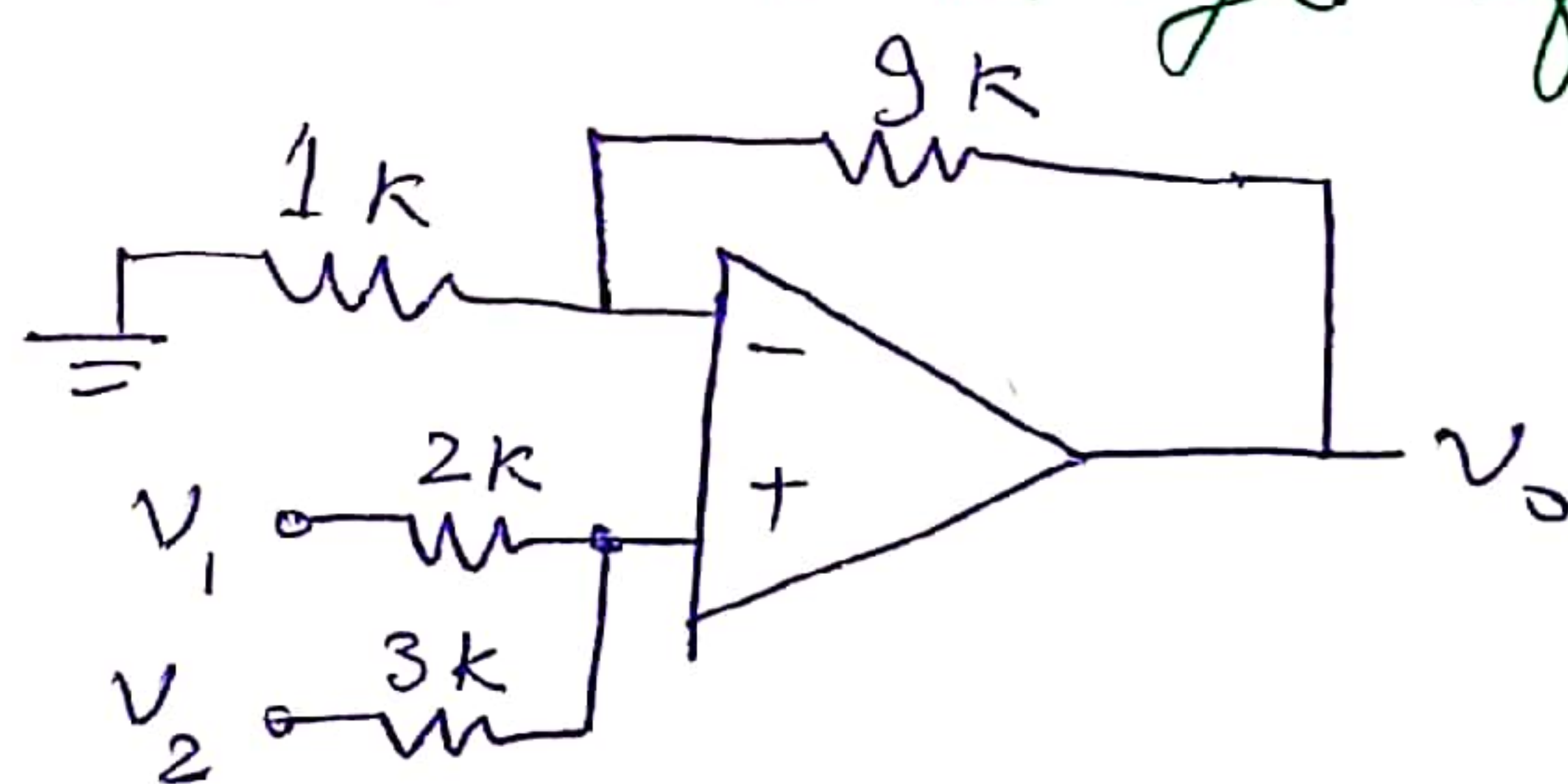
Example Find the output voltage of the shown circuit-



(1) Using superposition principle

$V_1$  &  $V_2$  applied individually one at a time

Only  $V_1$

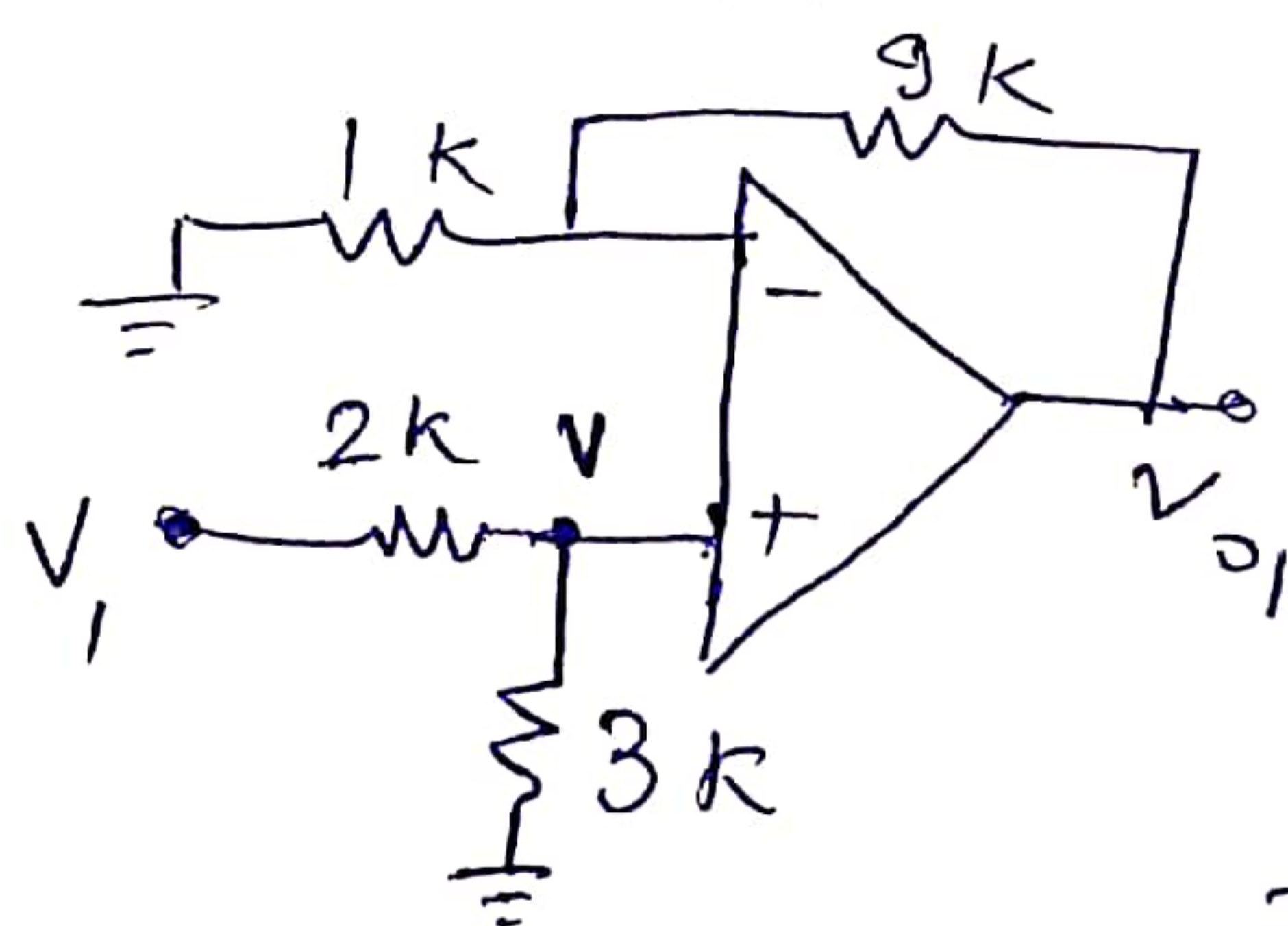


using voltage divider rule,  $V = \frac{3}{2+3} V_1$

$$V = \frac{3}{5} V_1$$

from (1),  $V_{o1} = \left( 1 + \frac{9k}{1k} \right) V = 10 \times \frac{3}{5} V_1 = 6V_1$

Only  $V_2$

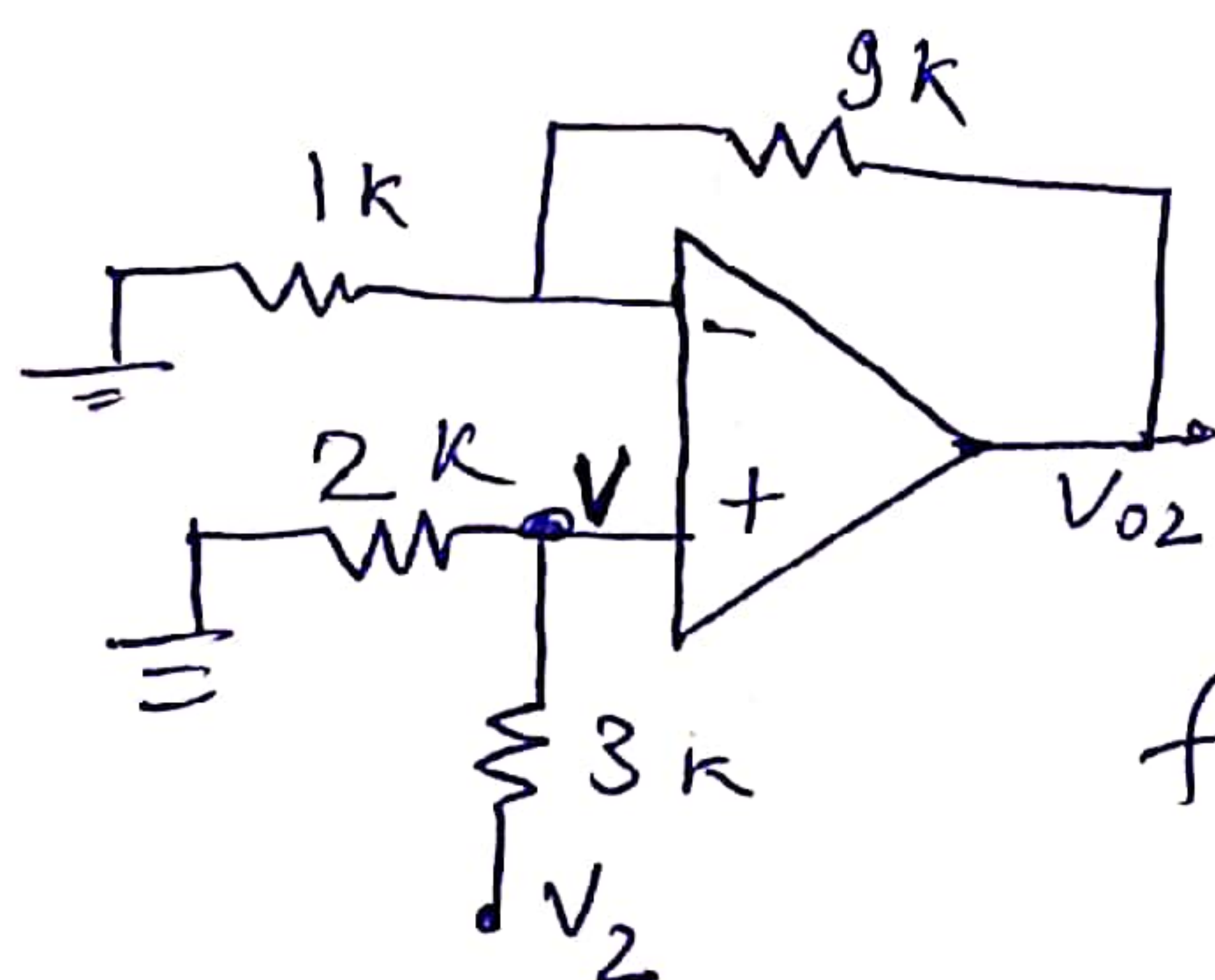

using voltage divider rule,  $V = \frac{2}{2+3} V_2 = \frac{2}{5} V_2$

from (1),  $V_{o2} = \left( 1 + \frac{9k}{1k} \right) V = 10 \times \frac{2}{5} V_2 = 4V_2$




The overall output voltage

$$V_o = V_{o1} + V_{o2}$$

$$V_o = 6V_1 + 4V_2$$

(11) Using Nodal eqn.

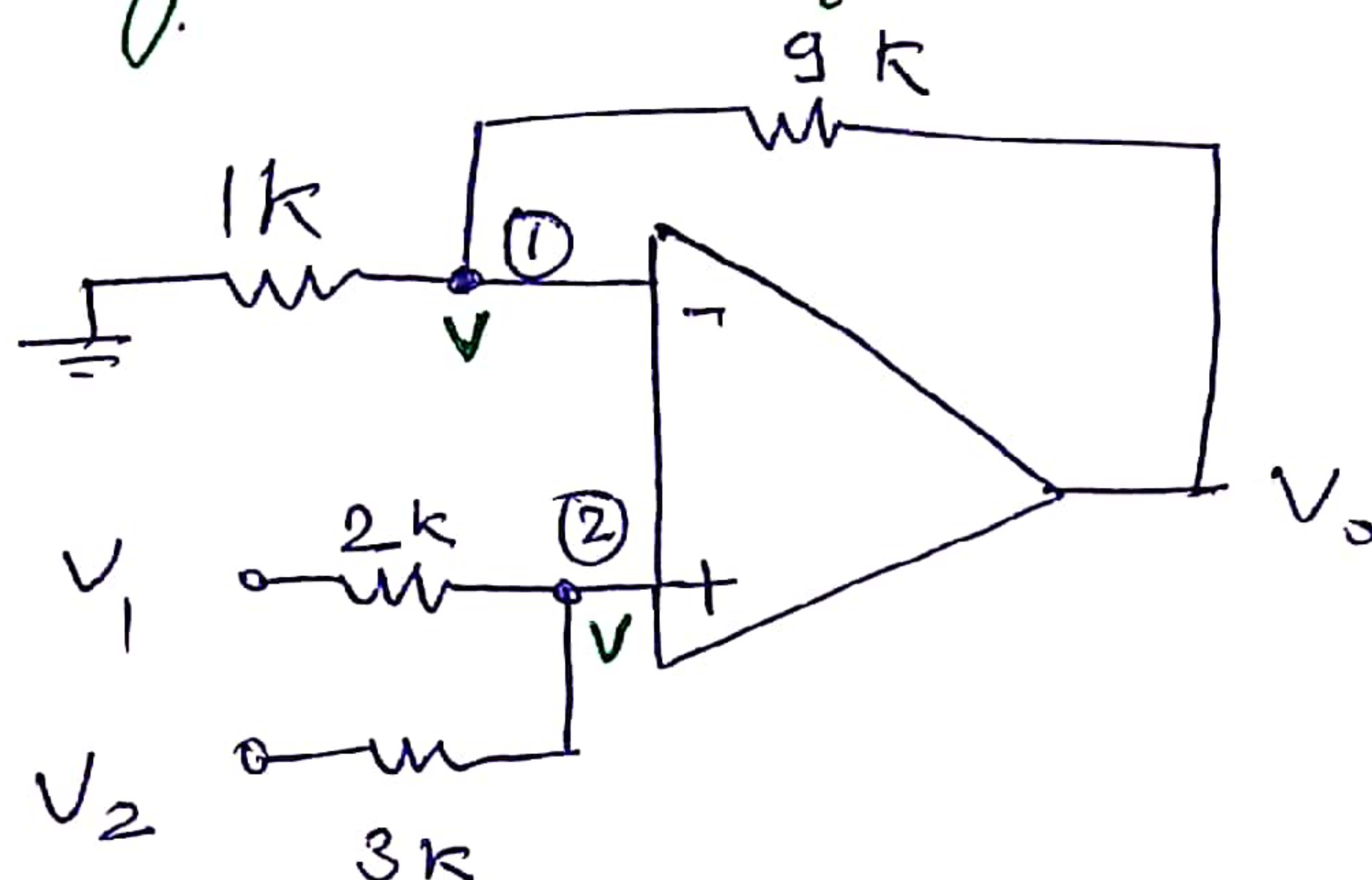

due to V.S.C, the voltages at both nodes ① & ② are same, Assume it to be  $V$

• Nodal eqn at ①

$$V \left( 1 + \frac{1}{9} \right) = \frac{V_o}{9}$$

$$V_o = 10V$$

$$10V = V_o \quad \text{--- (1)}$$

Nodal eqn at ②

$$V \left( \frac{1}{2} + \frac{1}{3} \right) = \frac{V_1}{2} + \frac{V_2}{3}$$

$$\frac{5}{6} V = \frac{V_1}{2} + \frac{V_2}{3} \quad \text{--- (2)}$$

• Dividing (1) by (2),


$$\frac{10V}{5/6 V} = \frac{V_o}{\frac{V_1}{2} + \frac{V_2}{3}}$$

$$\Rightarrow V_o = 12 \left( \frac{V_1}{2} + \frac{V_2}{3} \right)$$

$$V_o = 6V_1 + 4V_2$$



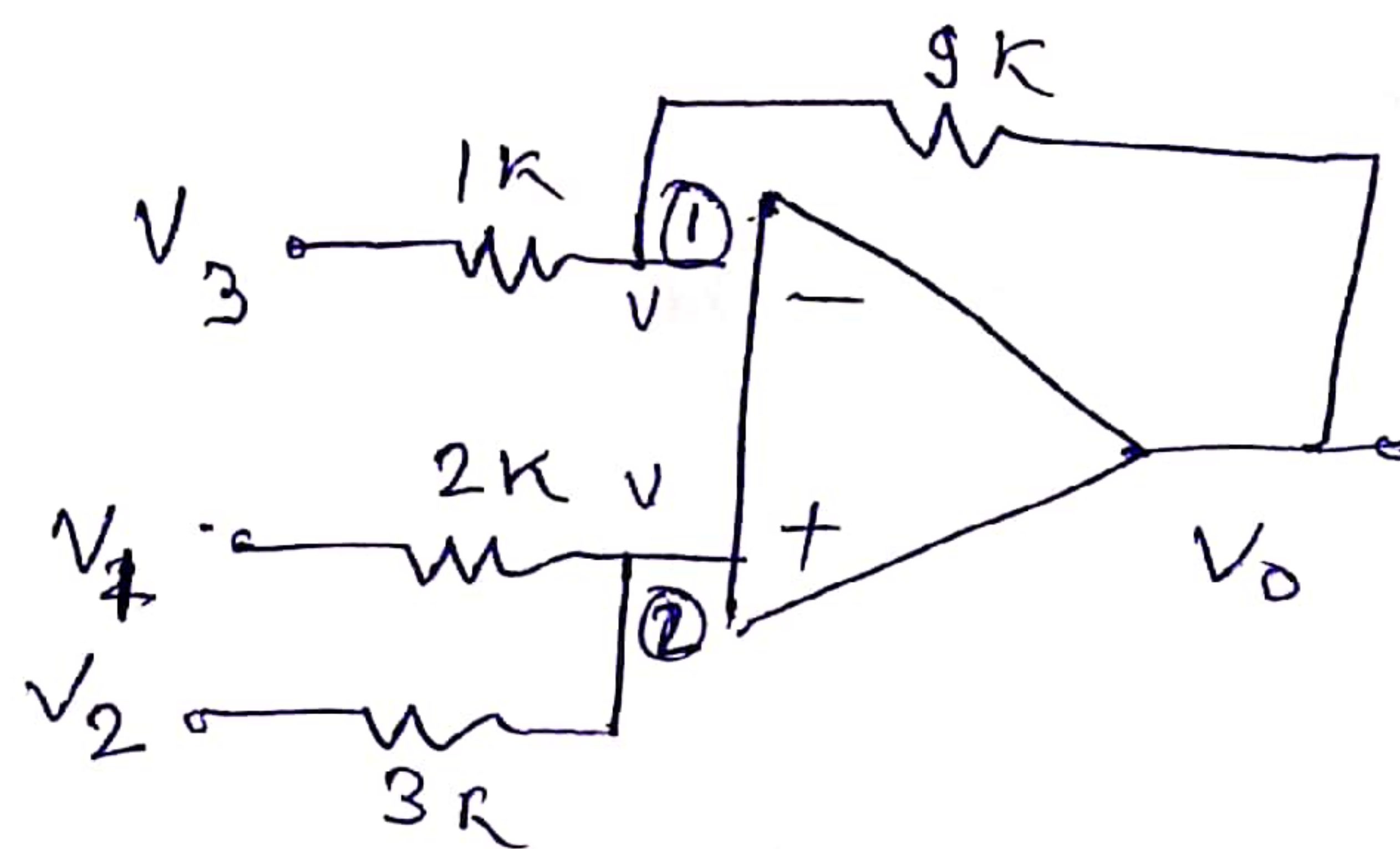Ex In the prev. example, determine  $v_o$  if  $1\text{ k}$  resistor is connected to  $V_3$  instead grounded.



using nodal eqn.

at Node ①,

$$v \left( 1 + \frac{1}{9} \right) = \frac{V_3}{1} + \frac{V_o}{9}$$

$$10v = 9V_3 + V_o \quad \text{--- (1)}$$

at Node ②, eqn remain the same

$$\frac{5}{6}v = \frac{V_1}{2} + \frac{V_2}{3} \quad \text{--- (2)}$$

Dividing (1) by (2)

$$\frac{10v}{5/6v} = \frac{9V_3 + V_o}{\frac{V_1}{2} + \frac{V_2}{3}}$$

$$12 \left( \frac{V_1}{2} + \frac{V_2}{3} \right) = 9V_3 + V_o$$

$$\boxed{V_o = 6V_1 + 4V_2 - 9V_3}$$

# Here we have an important observation, the weighted summer now have a negative weight as we can see.


The we can implement a negative  $k$  by applying any input voltage at non-inverting terminal as in the given example.


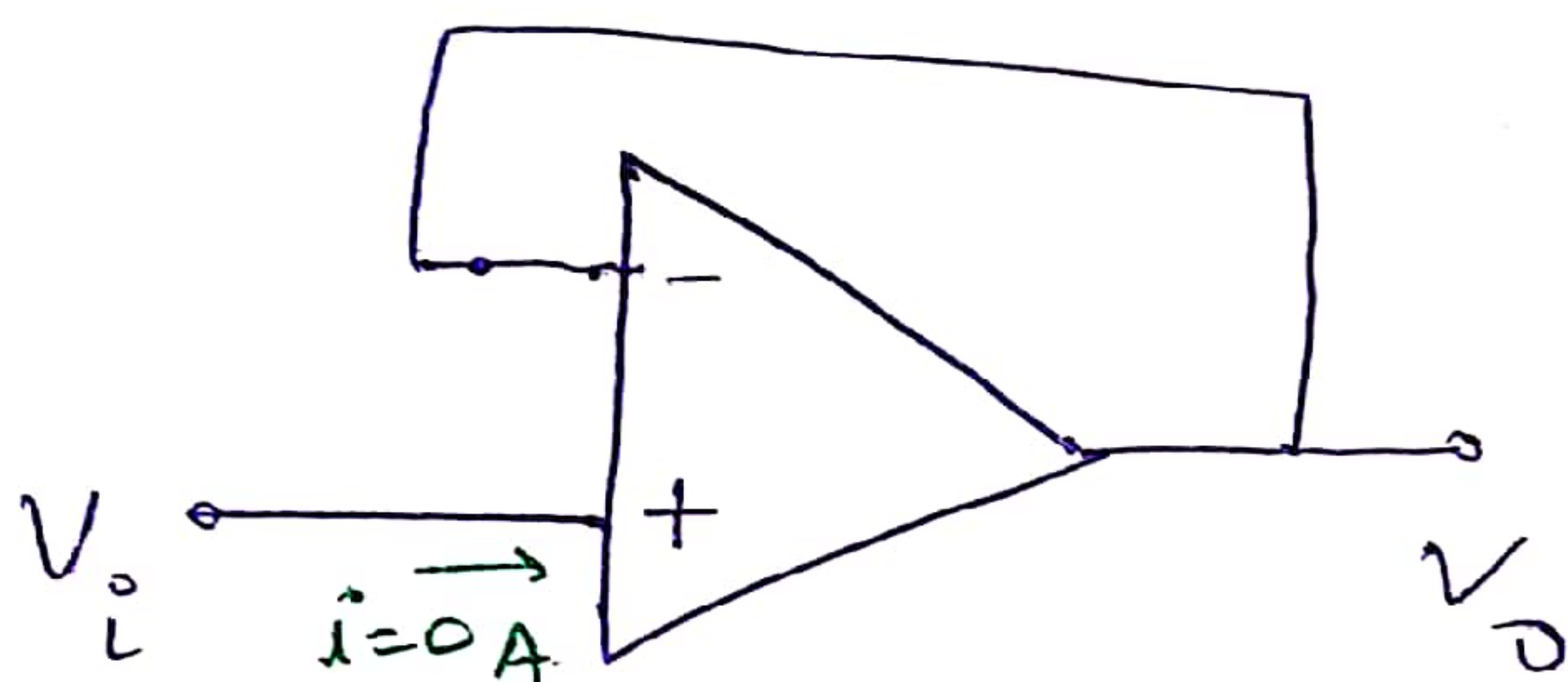
## Unity-gain Amplifier / Voltage Follower :-

Unity gain amplifier or buffer amplifier is used to connect a source with high impedance to a low impedance load without causing any voltage amplification.

Therefore it does not provide any voltage gain rather, it is mainly used as an impedance transformer.



due to virtual short circuit

$$V_o = V_i$$

$$\frac{V_o}{V_i} = 1$$

Voltage  
Gain is  
Unity

Output just follows the input, that is why it is called voltage follower

Input Impedance  $R_{in} = \infty$

Output Impedance  $R_{out} = 0$