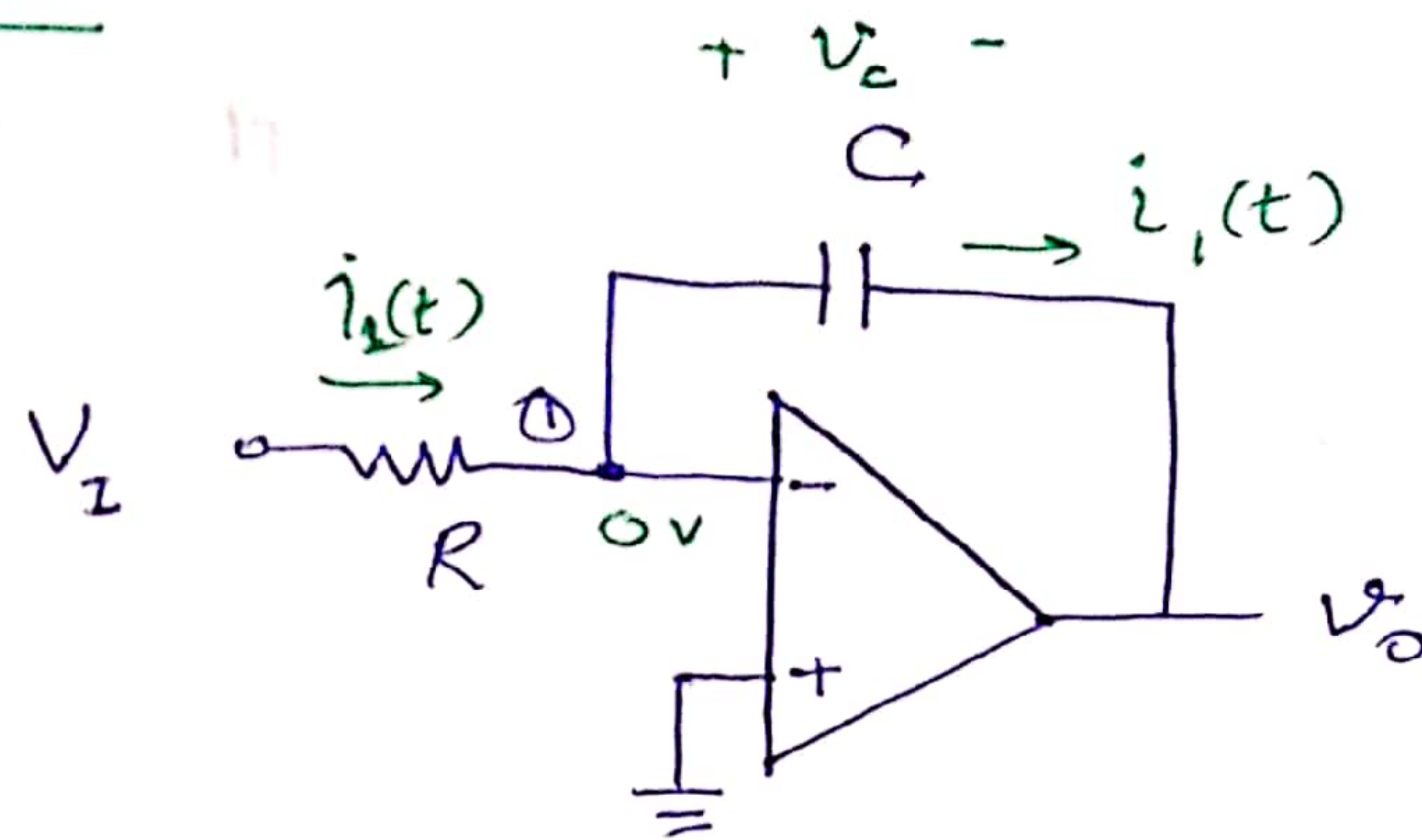


Opamp Integrator



Inverting Integrator Configuration

writing nodal equation at ①

$$0\left(\frac{1}{R} + sC\right) = \frac{V_i}{R} + V_o(sC)$$

Voltage gain

$$\boxed{\frac{V_o}{V_i} = -\frac{1}{sRC}}$$

(freq. domain)

capacitor impedance

$$X_C = \frac{1}{j\omega C}$$

$$X_C = \frac{1}{sC}$$

$$(s = j\omega)$$

for physical freq., $s = j\omega$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega RC}$$

Magnitude: $\left|\frac{V_o}{V_i}\right| = \frac{1}{\omega RC}$

Phase: $\phi = +90^\circ$

[RC is also known as
Integrator time constant]

At $\omega \cdot \left|\frac{V_o}{V_i}\right| = 1$, $\boxed{\omega = \frac{1}{RC}}$

known as integrator frequency

Output voltage in time domain:

if $i_i(t)$ be the current flowing through R, the same will also flow through C.

$$i_i(t) = \frac{V_i(t)}{R} \quad \text{---(1)}$$

Charge_{stored} on capacitor, if from 0 to t

$$Q = \int_0^t i_i(t) dt$$

Capacitor voltage, $V_c(t) = \frac{1}{C} \int_0^t i_i(t) dt$

(capacitor principle)

$$V = \frac{Q}{C}$$

but ^{here} $V_o = -V_c$

$$\therefore V_o(t) = -\frac{1}{C} \int_0^t i_c(t) dt$$

$$V_o(t) = -\frac{1}{RC} \int_0^t V_i(t) dt$$

Using (i)


DC problem in integrators

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{j\omega C} = \frac{1}{\omega RC}$$

at dc ($\omega=0$), $\frac{V_o}{V_i} \Rightarrow \infty$

The gain becomes infinite and opamp saturates. To avoid this problem, generally, a feedback resistor, R_F is connected in parallel with C .
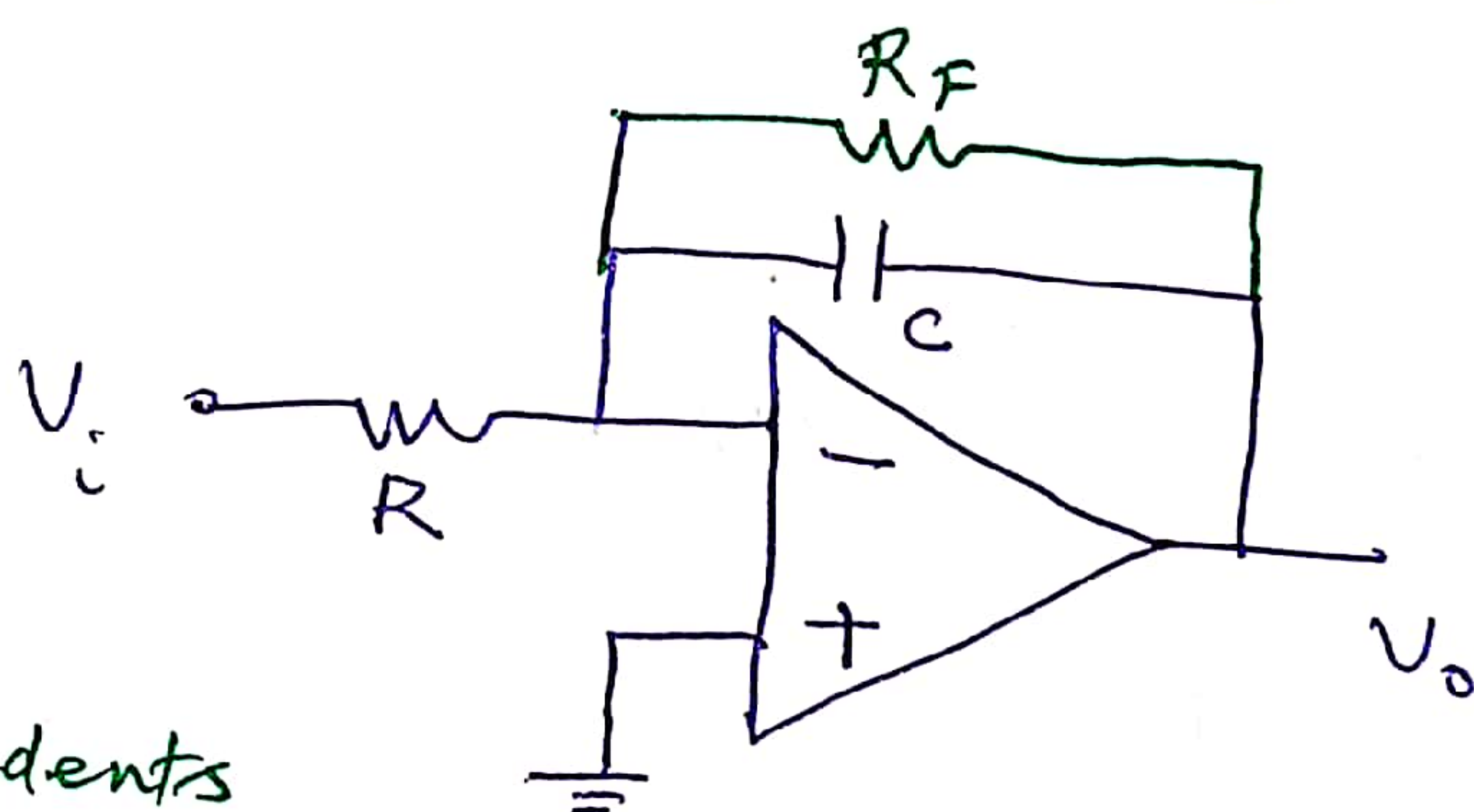
$$\frac{V_o}{V_i} = -\frac{R_F/R}{1 + sRC_F}$$




⇒ Derivation is left for students

In this case,

at dc ($\omega=0$), capacitor behaves as open circuit and structure simply becomes an inverting amplifier with voltage gain

$$\frac{V_o}{V_i} = -R_F/R$$

Opamp Differentiator :-

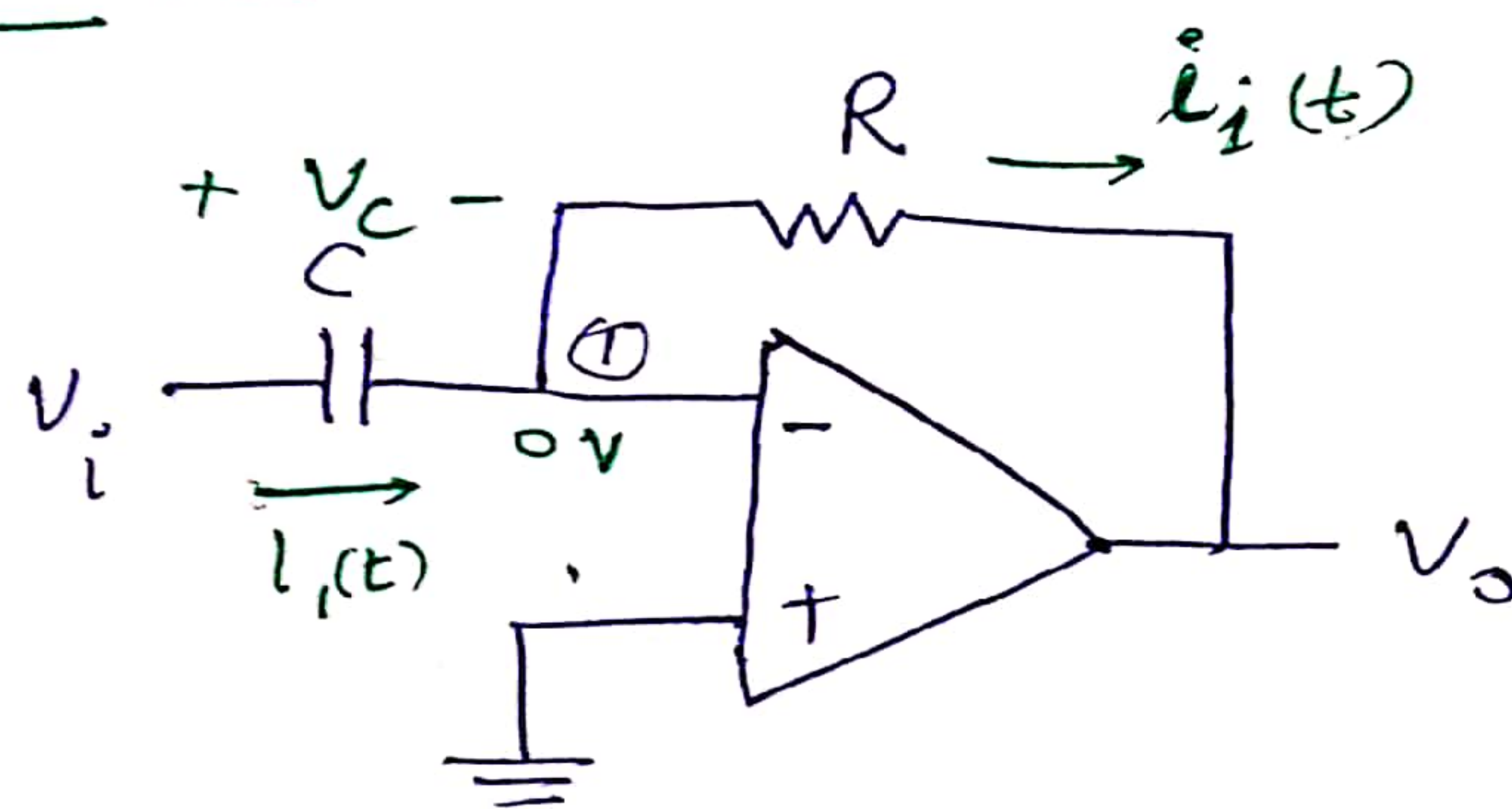

Interchanging the position of R & C results in an opamp differentiator

Writing nodal equation at (1),

$$0 \left(\frac{1}{R} + sC \right) = V_i(sC) + V_o \times \frac{1}{R}$$

$$\Rightarrow \frac{V_o}{R} = -V_i sC$$

$$\boxed{\frac{V_o}{V_i} = -sRC}$$

for physical frequency $s = j\omega$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -j\omega RC$$

magnitude, $\left| \frac{V_o}{V_i} \right| = \omega RC$

Phase, $\phi = -90^\circ$

At $|V_o/V_i| = 1$

$$\boxed{\omega = \frac{1}{RC}}$$

known as differentiator freq.

≠ Output voltage in time domain:

for capacitor, $V_c(t)$ with voltage $V_c(t)$

$$I_c(t) = C \frac{dV_c(t)}{dt}$$

here
but $V_c(t) = V_i(t)$

(capacitor principle)

$$i_1(t) = C \frac{dV_i(t)}{dt}$$

Same $i_1(t)$ will also flow through R ,

$$V_o(t) = -R i_1(t)$$

$$V_o(t) = -RC \frac{dV_i(t)}{dt}$$