


HA-II

Roll date of submission  $\rightarrow$  20/11/19.

Q. ~~Derive~~ Derive the o/p voltage expression for 2-input non-inverting summing amplifier.

Q.2 calculate the output voltage for  $R_1 = 33k\Omega$ ,  $R_2 = 22k\Omega$ ,  $R_3 = 12k\Omega$ ,  $R_f = 68k\Omega$ ,  $V_1 = 0.2V$ ,  $V_2 = -0.5V$  and  $V_3 = 0.8V$


Assume Ideal operational amplifier.

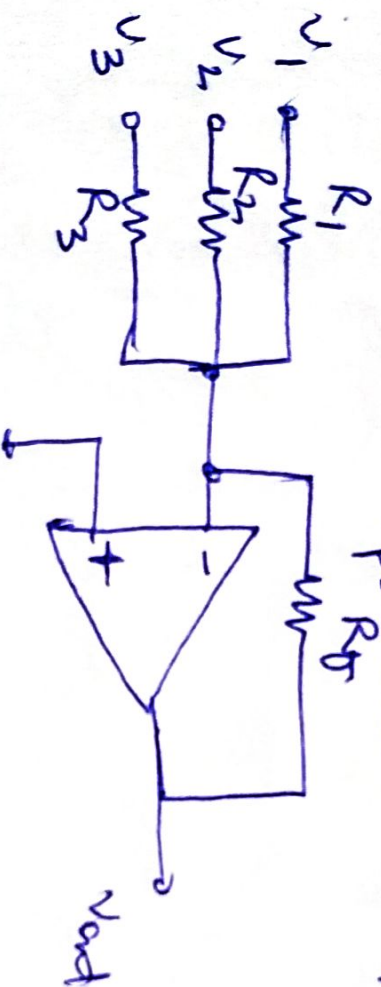


Q.3 Design a weighted summer using ~~two~~ opamps and resistors that implements the following function:

$$V_o = -3V_1 - 4V_2$$

51. Calculate the current through the  $2.2\text{-k}\Omega$  load in the circuit of Fig. 4.147.
52. For the circuit of Fig. 4.148, calculate the current  $I$ .

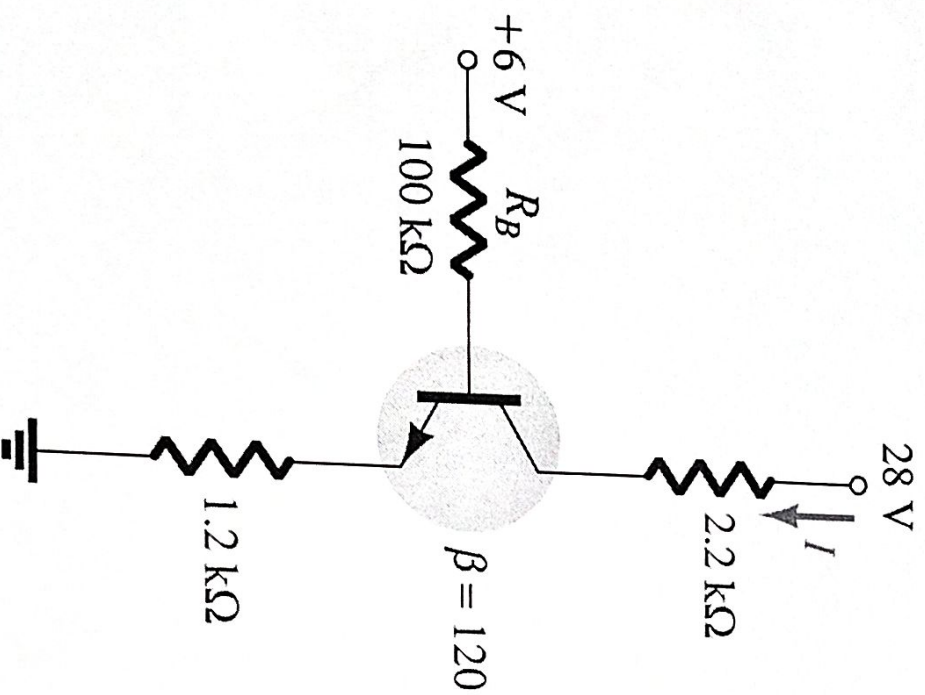

**FIG. 4.147**  
Problem 51.

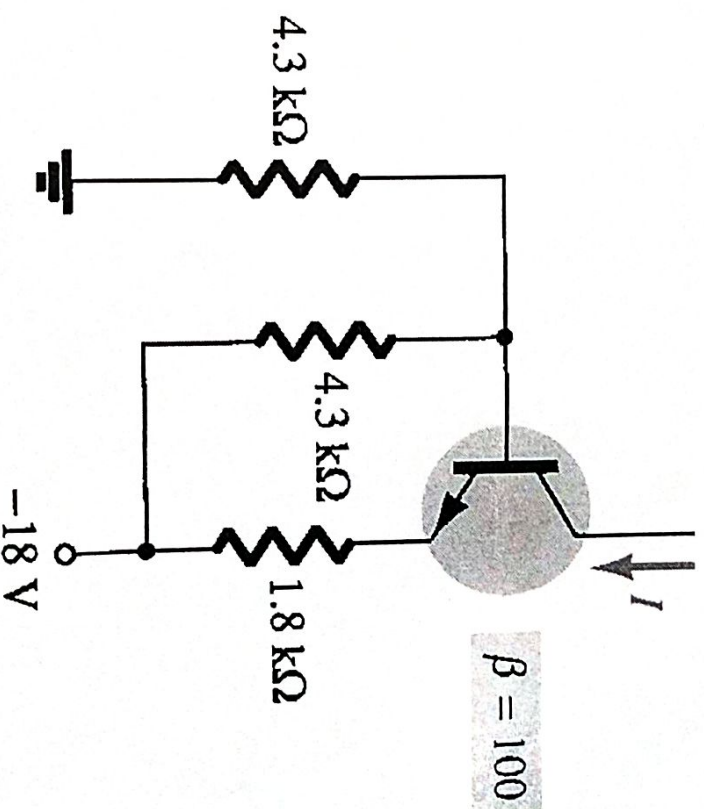

**FIG. 4.148**  
Problem 52.



- \*43. a. Design the network of Fig. 2.187 to maintain  $V_L$  at 12 V for a load variation ( $I_L$ ) from 0 mA to 200 mA. That is, determine  $R_S$  and  $V_Z$ .  
 b. Determine  $P_{Z \max}$  for the Zener diode of part (a).
- \*44. For the network of Fig. 2.188, determine the range of  $V_i$  that will maintain  $V_L$  at 8 V and not exceed the maximum power rating of the Zener diode.

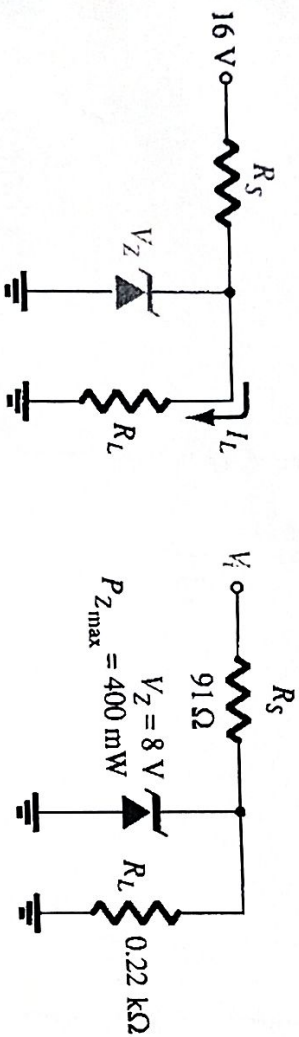


FIG. 2.187

FIG. 2.188

38. Sketch  $v_o$  for each network of Fig. 2.182 for the input shown.

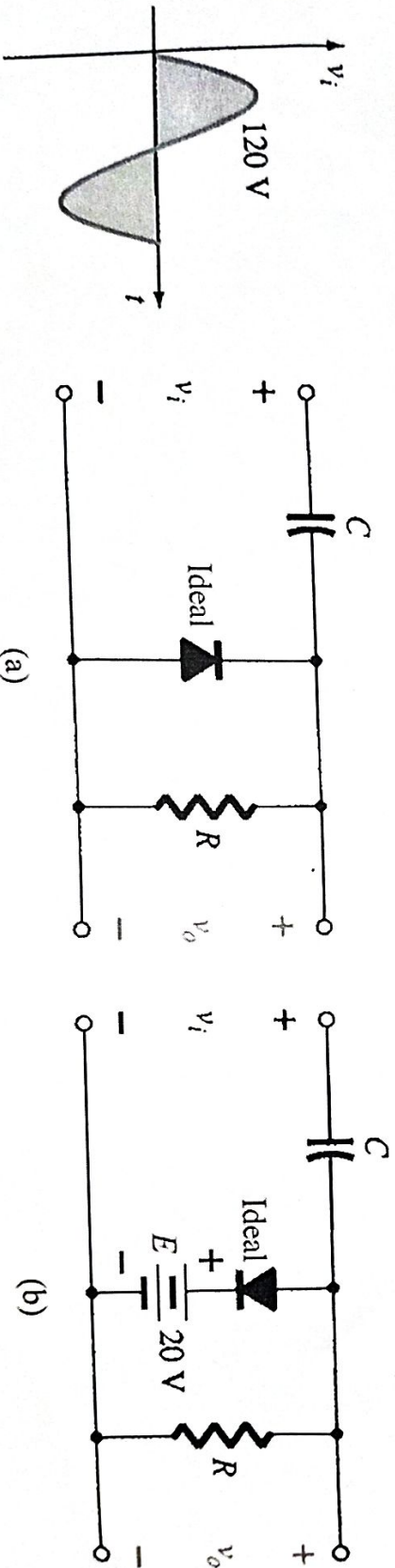


FIG. 2.182

Problem 38.