



COC2070

ASSIGNMENT 4

NAME:- MOHD. ZAID ALI

FACULTY NO:- 19COB103

ENROLL. NO:- GL3125

Q1

Assignment 4

Question 1: Design a simple Computer with following instructions:

operation Code	Mnemonic	Description	Function
00000001	ADD R	Add R to A	$A \leftarrow A + R$
00000010	ADI OPRD	Add opr to A	$A \leftarrow A + OPRD$
00000011	ADA ADRS	Add direct to A	$A \leftarrow A + M[ADRS]$

Soln

OP code fetch: (same for all instructions):

t_0 $MAR \leftarrow PC$ (program code)
 t_1 $MBR \leftarrow M[MAR]$
 t_2 $IR \leftarrow MBR$

$q_1 \text{ high} \left\{ \begin{array}{l} q_1 t_3 \\ q_1 t_4 \end{array} \right.$ $A \leftarrow A + R.$ (ADD R)

$q_3 \text{ high} \left\{ \begin{array}{l} q_2 t_3 \\ q_2 t_4 \\ q_2 t_5 \end{array} \right.$
 $MAR \leftarrow PC$
 $MBR \leftarrow M[MAR]$ $PC \leftarrow PC + 1$ (ADI OPRD)
 $A \leftarrow A + MBR.$ $T \leftarrow 0$ reset timer.

$q_3 \text{ high} \left\{ \begin{array}{l} q_3 t_3 \\ q_3 t_4 \\ q_3 t_5 \\ q_3 t_6 \\ q_3 t_7 \end{array} \right.$
 $MAR \leftarrow PC$
 $MBR \leftarrow M[MAR]$ $PC \leftarrow PC + 1$ (ADA ADRS)
 $MAR \leftarrow MBR$
 $A \leftarrow A + M[ADRS]$ $T \leftarrow 0$ reset timer.
 $MBR \leftarrow M[MAR]$
 $A \leftarrow A + MBR$ $T \leftarrow 0$ reset timer.

$$x_1 = t_0 + q_2 t_3 + q_3 t_3$$

$$MAR \leftarrow PC$$

$$x_2 = q_3 t_4$$

$$MAR \leftarrow MBR$$

$$x_3 = t_1 + q_2 t_4 + q_3 t_4$$

$$PC \leftarrow PC + 1$$

$$MBR \leftarrow M[MAR]$$

$$x_4 = q_3 t_4 + q_2 t_4$$

$$MBR \leftarrow A + MBR$$

$$x_5 = q_2 t_5 + q_3 t_7$$

$$A \leftarrow A + R$$


$$x_6 = q_1 t_3$$

$$T \leftarrow 0$$

$$x_7 = x_5 + x_6$$

$$IR \leftarrow MBR$$

$$x_8 = t_2$$

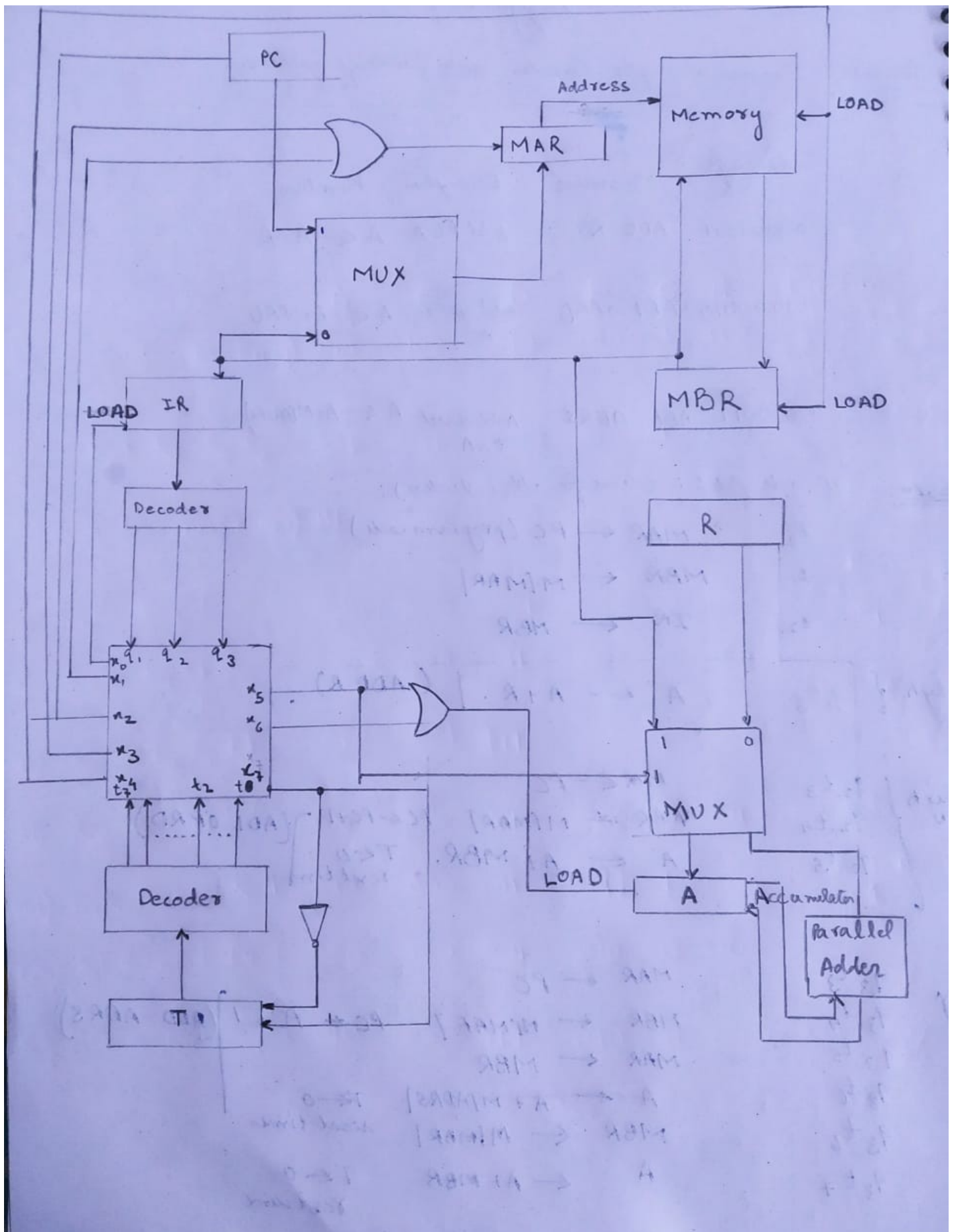

Q2

Q2. Find the control words for the following microoperations and specify the function being carried out.

Microoperation	A	B	D	F	C	H	Function
i) $R_2 \leftarrow \text{clc}(R_2 + R_4 + 1)$	010	100	010	010	1	110	Add R_2, R_4 & carry and circulate whole to left.
ii) $-R_3 + R_5 \equiv R_5 - R_3$ $\equiv \bar{R_3}$	101	011	000	010	1	000	Subtract R_3 from R_5
iii) $\text{Output} \leftarrow \text{shr}(R_7 - R_2 - 1)$ $\text{shr} = \lfloor \frac{R_7 - (R_2 + 1)}{2} \rfloor$	111	010	000	010	0	001	Shift right after sub. $(R_2 + 1)$ from R_7
iv) $R_1 \leftarrow \text{Input}$	000	000	001	000	0	000	Set Transfer Input to R_1
v) $R_3 \leftarrow \bar{R_4} + 1$ $\equiv -R_4$	100	000	011	000	0	000	Transfer 2's complement of R_4 to R_3
vi) $R_6 \leftarrow R_2 - R_1 + 1$ $= (R_2 + 1) - R_1$ $= (R_2 + 1) + (\bar{R_1} + 1)$	010	001	010	010	1	010	Subtraction with Borrow
vii) $R_5 \leftarrow 0$	000	000	101	000	0	011	Set R_5 to zero
viii) $R_3 \leftarrow R_2, C \leftarrow 1$	010	000	011	011	1	000	Set R_3 to R_2 with Carry 1
ix) $R_1 \leftarrow \text{Input} - R_4 - 1$	000	100	001	010	0	000	Subtract $(R_4 + 1)$ from Input. May Borrow as 1.
x) $R_7 \leftarrow \bar{R_6} + \text{Input}$	010	000	111	010	0	000	Add 1's complement and input & transfer to R_7